

Problem Set #2, EE part

Issue date: Nov. 14, 2020; Deadline: 23:59, Nov. 22, 2020


Student Name: _____ Student No.: _____

1. CMOS logic gate


Use the fundamental CMOS logic circuit units, such as NOT, AND, OR, to build a XOR gate

- Truth table and logic circuit (gate level) design. (10')


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

 

- CMOS-level implementation (15')

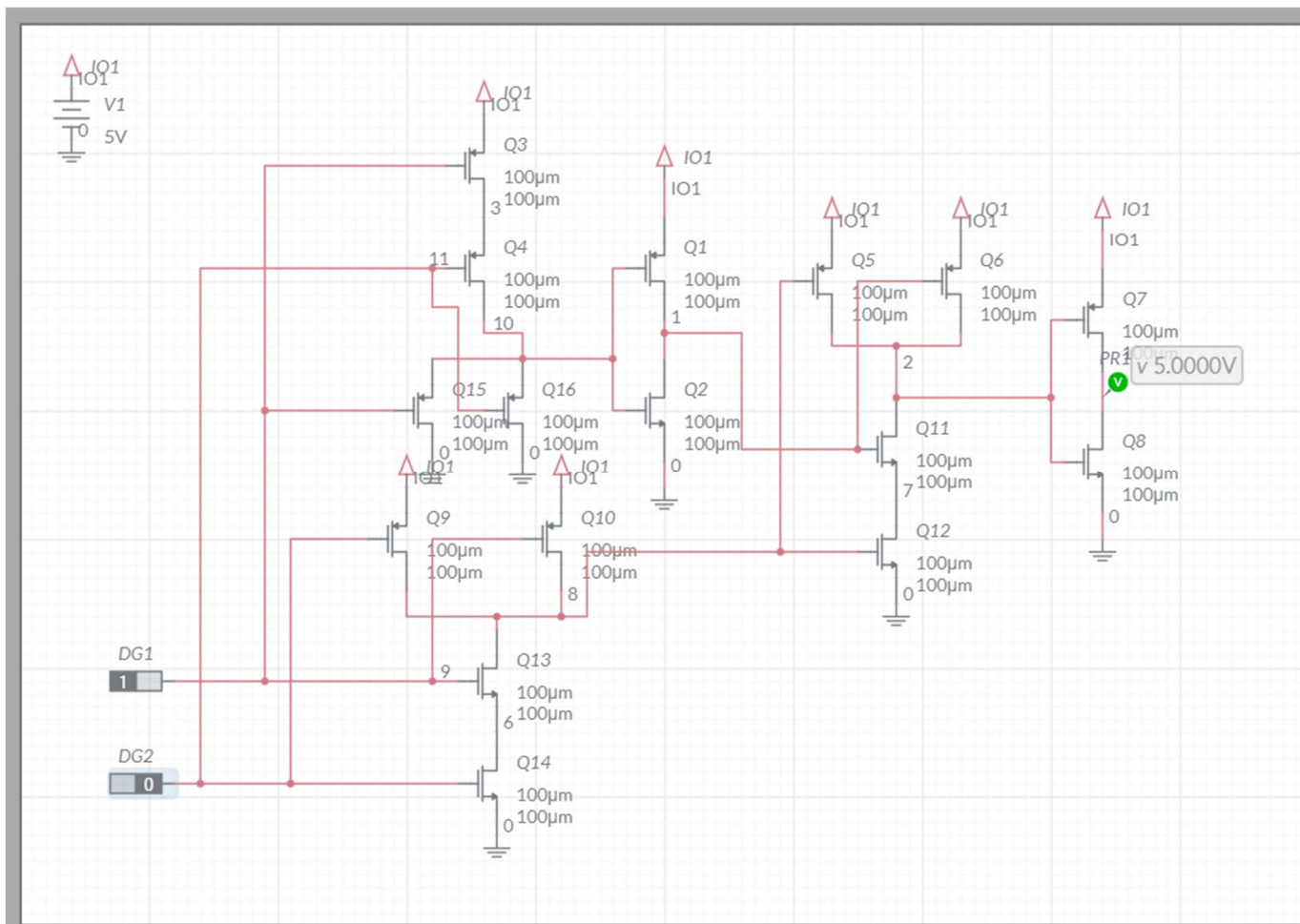

- Measurement results (5')

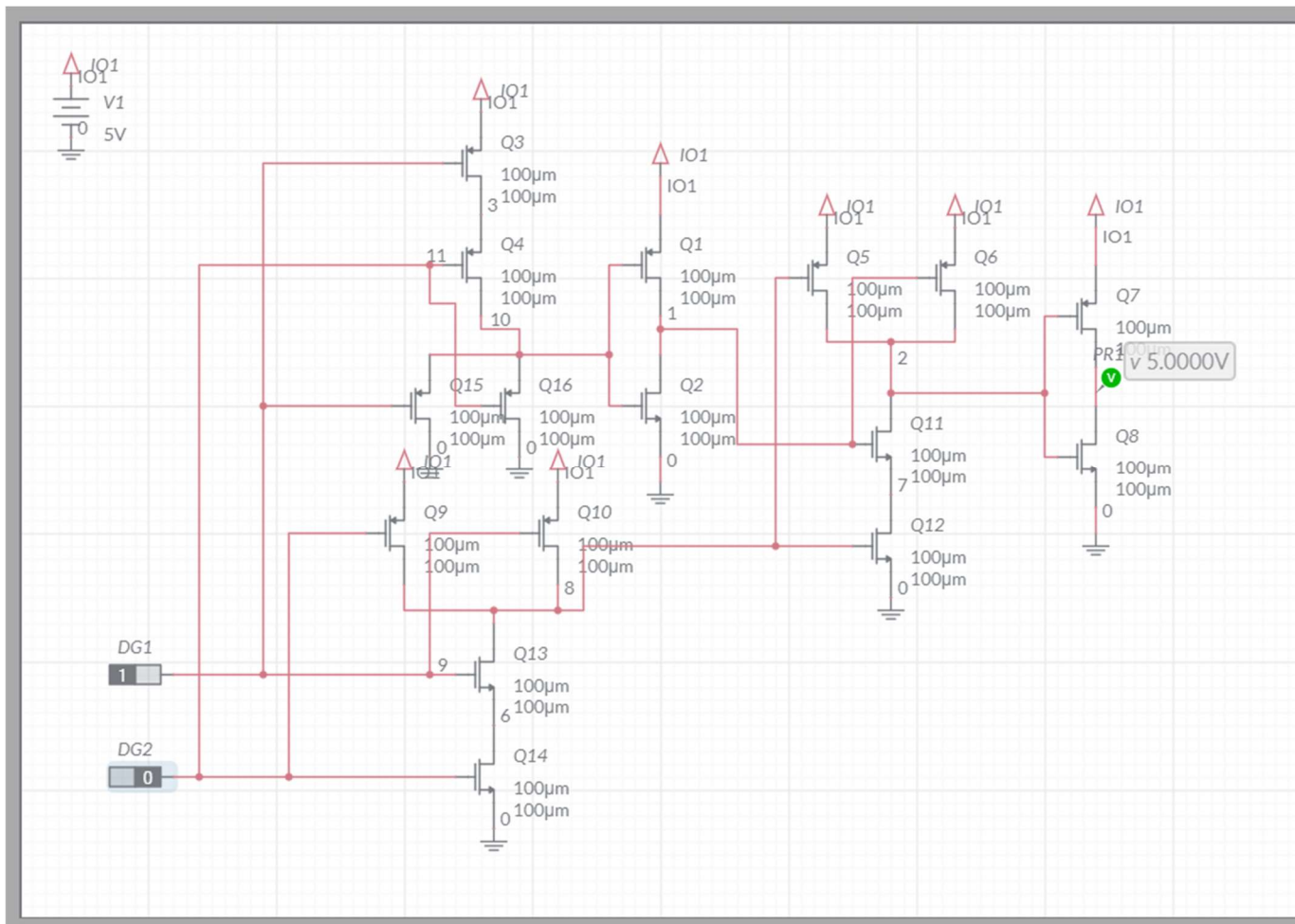

2. Combinational logic circuit exercises

- Write the Boolean equations in sum-of-products canonical form for each of the truth tables ($2^3 \times 5$)

a) $Y = \overline{A} \overline{B} + \overline{A} B + AB$

b) $Y = \overline{A} \overline{B} \overline{C} + ABC$

c) $Y = \overline{A} \overline{B} \overline{C} + \overline{A} B C + \overline{A} B \overline{C} + \overline{A} B C + ABC$

$$d) Y = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}CD + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D} + ABC\overline{D}$$

$$e) Y = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D} + \overline{A}BC\overline{D} + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D} + AB\overline{C}\overline{D} + ABC\overline{D}$$

- Simplify the logic using the K-map ($2^n \times 5$)

$$a) Y = A + \overline{B}$$

a)

B	0	1
A	1	0
0	1	0
1	1	1

$$b) Y = ABC + \overline{A}\overline{B}\overline{C}$$

b)

BC	00	01	11	10
A	1	0	0	0
0	1	0	0	0
1	0	0	1	0

$$c) Y = \overline{B}\overline{C} + AC + \overline{A}\overline{C}$$

c)

BC	00	01	11	10
A	1	0	0	1
0	1	0	0	1
1	1	1	1	0

$$d) Y = \overline{A}\overline{B} + AC\overline{D} + A\overline{B}\overline{D}$$

d)

CD	00	01	11	10
AB	1	1	1	1
00	1	1	1	1
01	0	0	0	0
11	0	0	0	1
10	1	0	0	1


$$e) Y = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D} + \overline{A}BC\overline{D} + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D} + AB\overline{C}\overline{D} + ABC\overline{D}$$

e)


CD	00	01	11	10
AB	1	0	1	0
00	1	0	1	0
01	0	1	0	1
11	1	0	1	0
10	0	1	0	1

- Implement the circuits in Multisim and test their performance (2' * 5)


a)


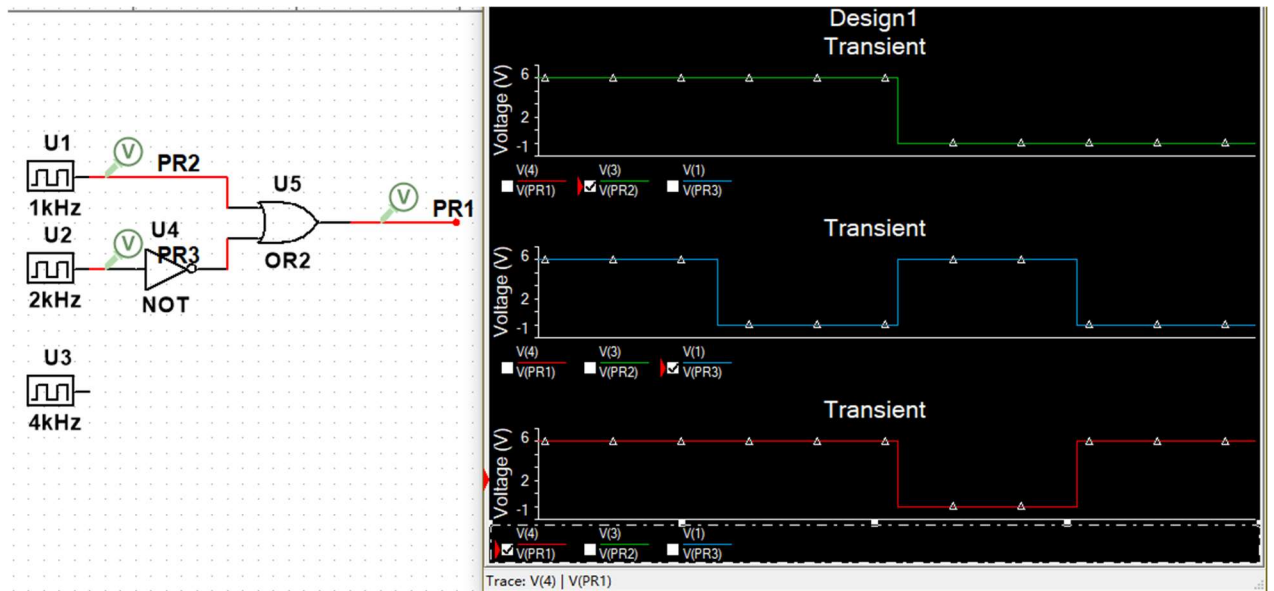


b)


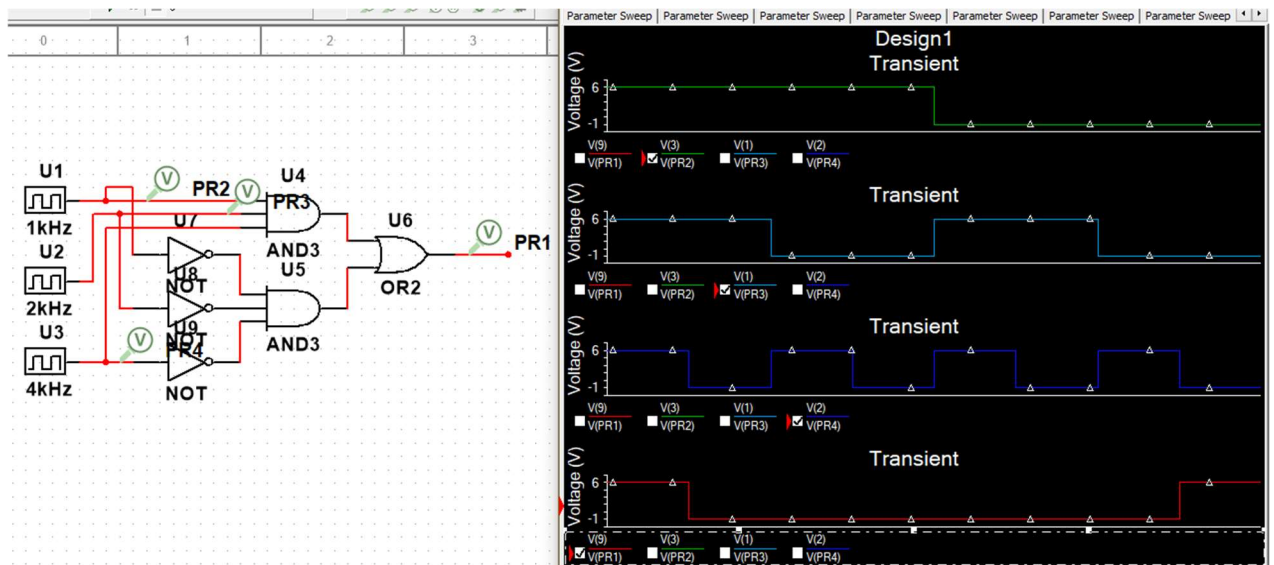


c)

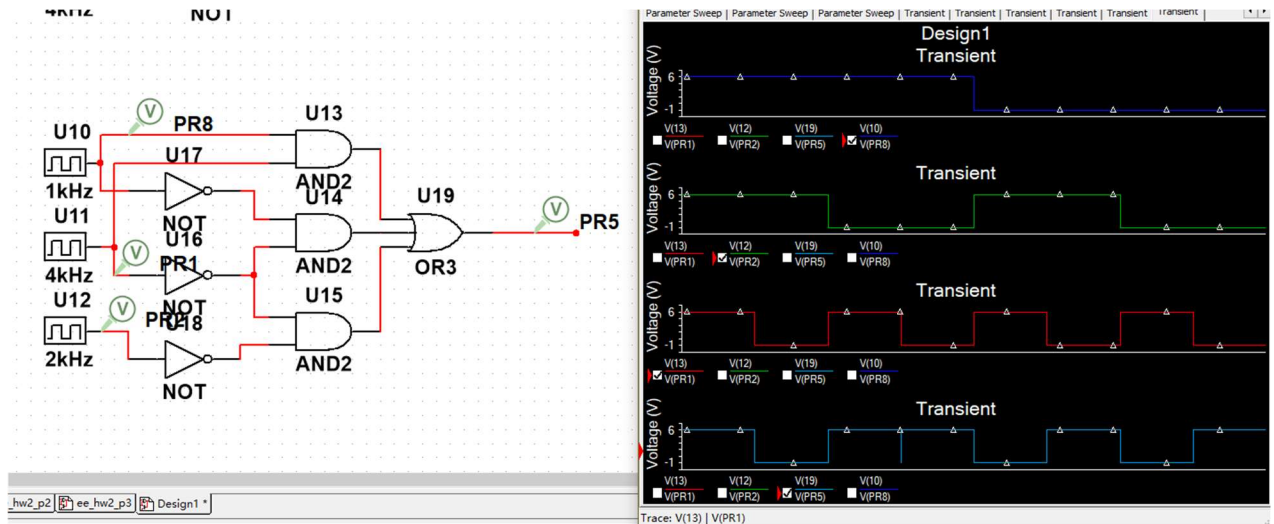

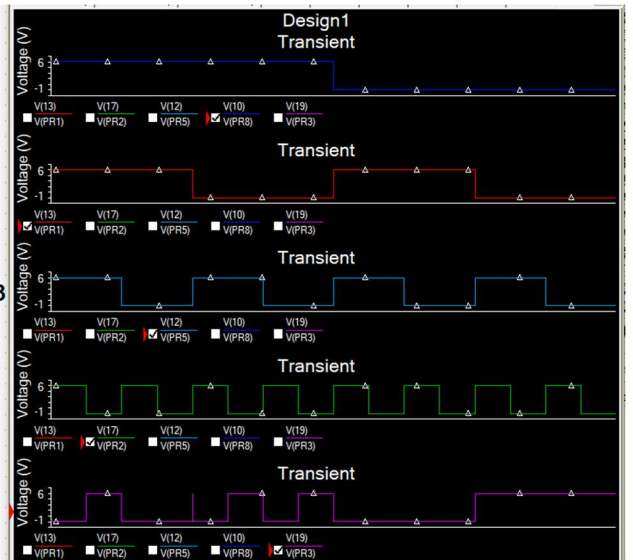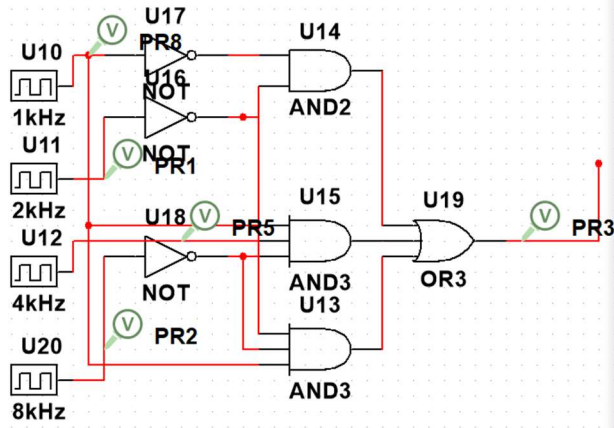

d)

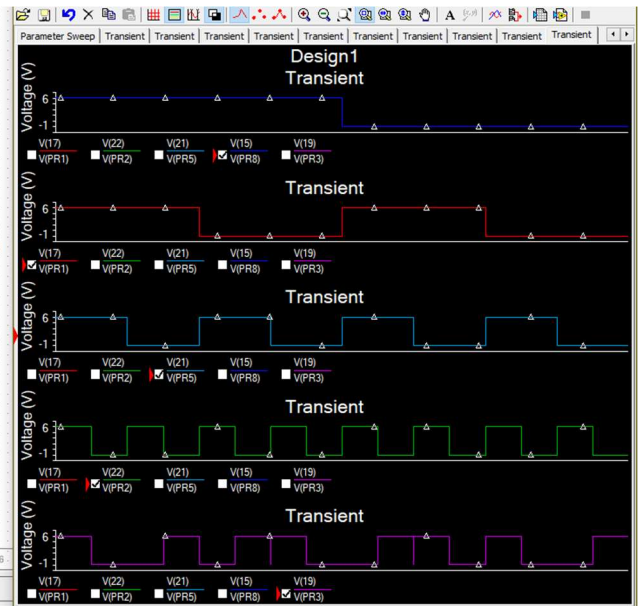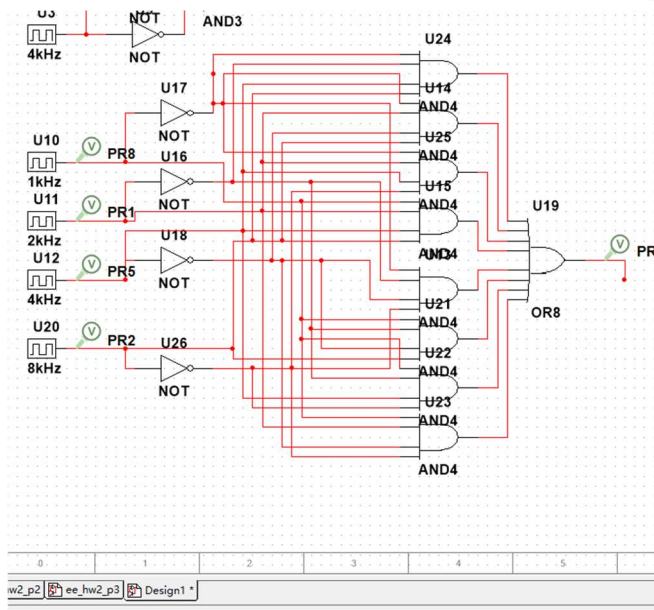

e)

(a)			(b)				(c)				(d)					(e)				
A	B	Y	A	B	C	Y	A	B	C	Y	A	B	C	D	Y	A	B	C	D	Y
0	0	1	0	0	0	1	0	0	0	1	0	0	0	0	1	0	0	0	0	1
0	1	0	0	0	1	0	0	0	1	0	0	0	0	1	1	0	0	0	1	0
1	0	1	0	1	0	0	0	1	0	0	0	0	1	0	0	0	1	0	0	0
1	1	1	0	1	1	0	0	0	1	1	0	0	0	0	0	0	1	0	0	0
			1	0	0	0	0	1	0	0	1	0	0	0	0	0	1	0	1	0
			1	0	1	0	0	1	0	1	0	0	0	0	0	0	1	1	0	1
			1	1	0	0	0	1	1	0	0	0	0	0	0	1	1	0	1	0
			1	1	1	1	1	1	1	1	1	1	1	1	0	1	1	1	1	1

3. Majority voting and 14-segment alphabet display

Referring to the majority voting system introduced in the lecture, design a logic circuit with Multisim and show the voting result with a 14-segment display as follows (T for Trump and B for Biden).

- Show the design procedures and final circuit schematic. (15')
- 1. Connect pin CA to Vcc.
- 2. Notice that for any display, LED [A J M] is **always on**. Connect them to GND.
- 3. When Biden wins, LED [B C G2 D] should be on. Since we use **common anode** alphanumeric display, we should have low input level for these pins.
- 4. According to 3, make the truth table. (1 for Trump and 0 for Biden)


A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- 5. Use K-map to simplify.




	BC	00	01	11	10
A					
0		0	0	1	0
1		0	1	1	1

We got: $Y = AB + AC + BC = \overline{AB} \overline{BC} \overline{AC}$

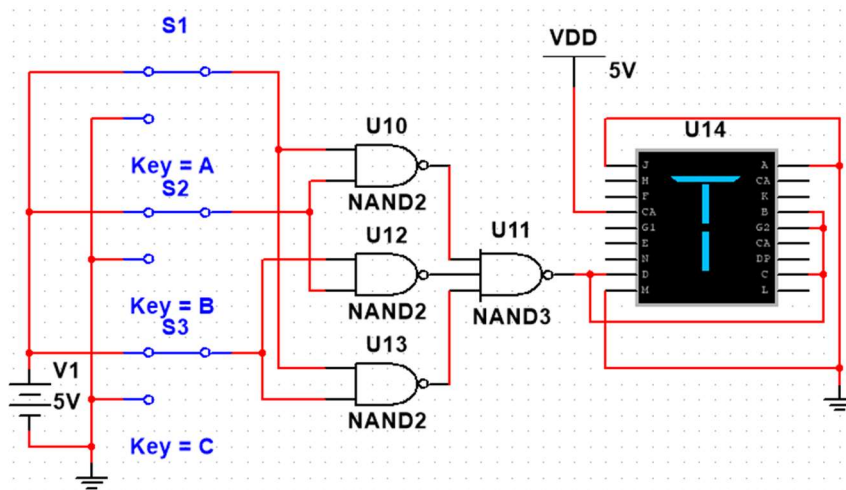
6. We have got the logic equation. Now create the circuit according to it.



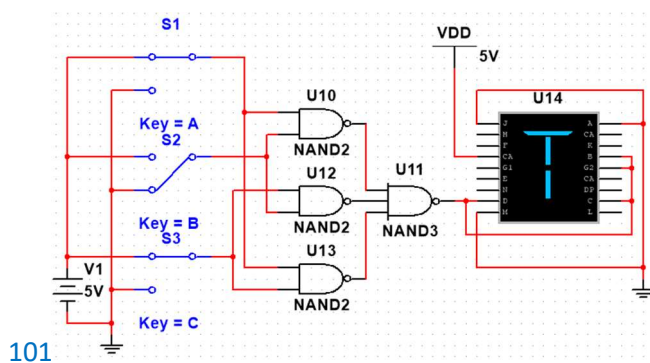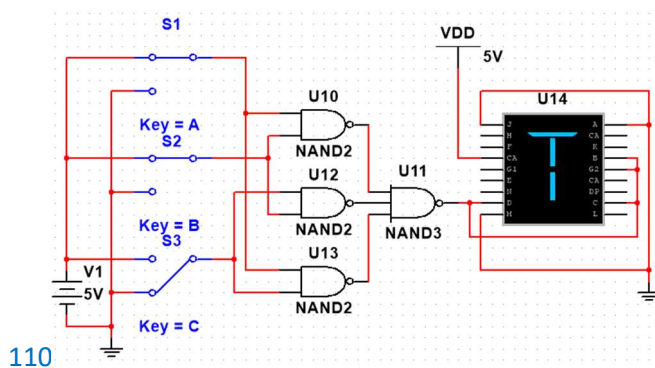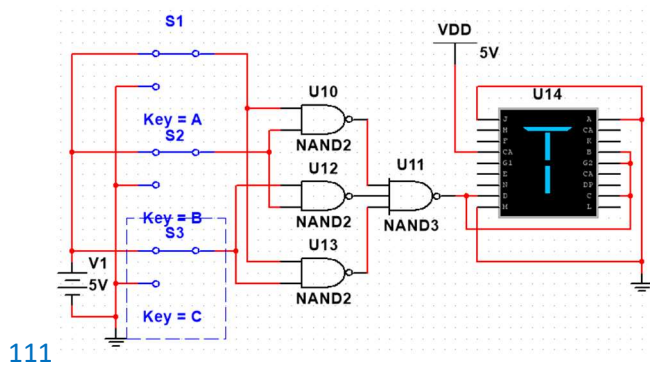
- Show the result pictures of six input conditions. (5')




100

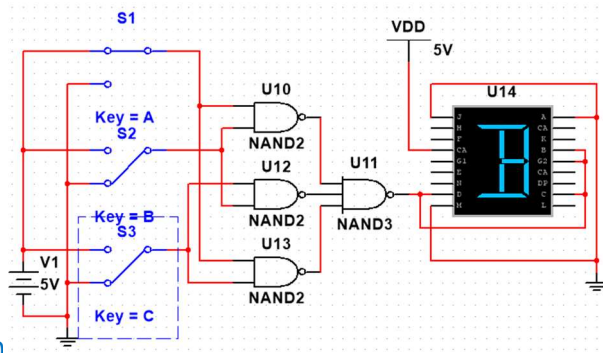


011

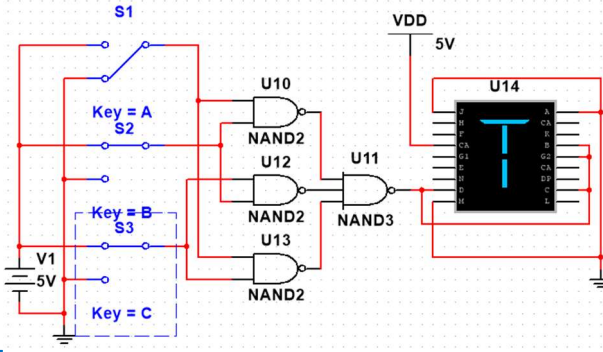


010

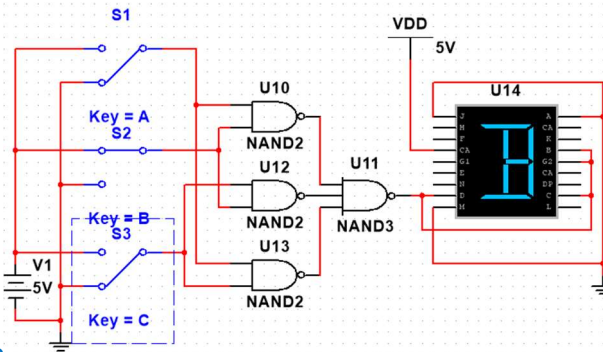


001

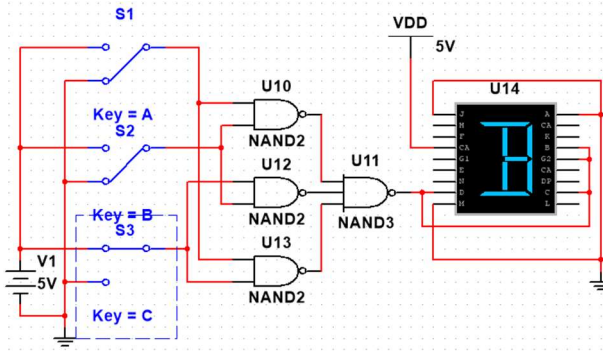




000

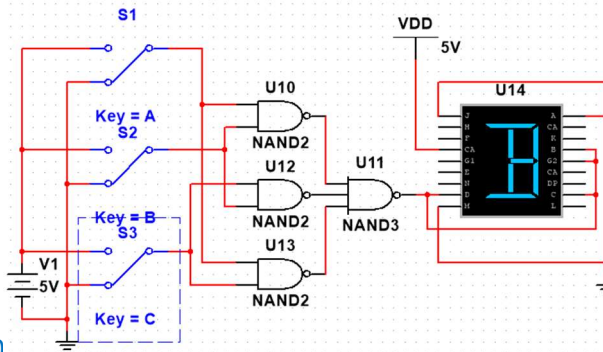



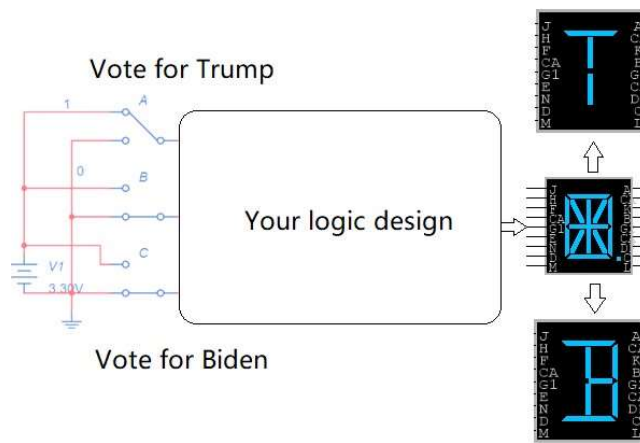


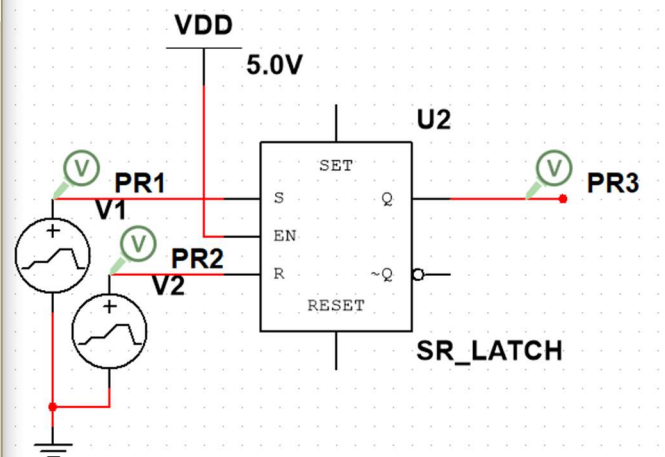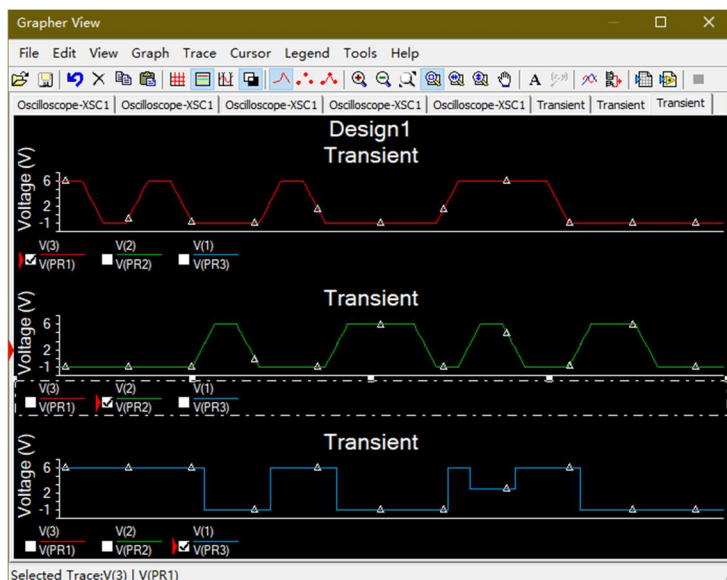 4. Sequential logic circuit exercises

- Given the input waveforms shown in the following figure, sketch the output, Q, of an SR latch. Check it out with Multisim and show the schematic and simulation result. (10')



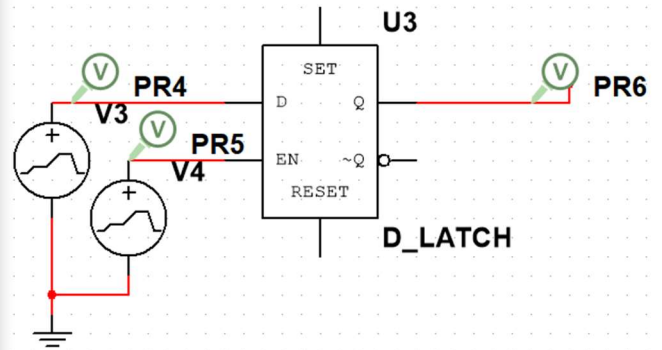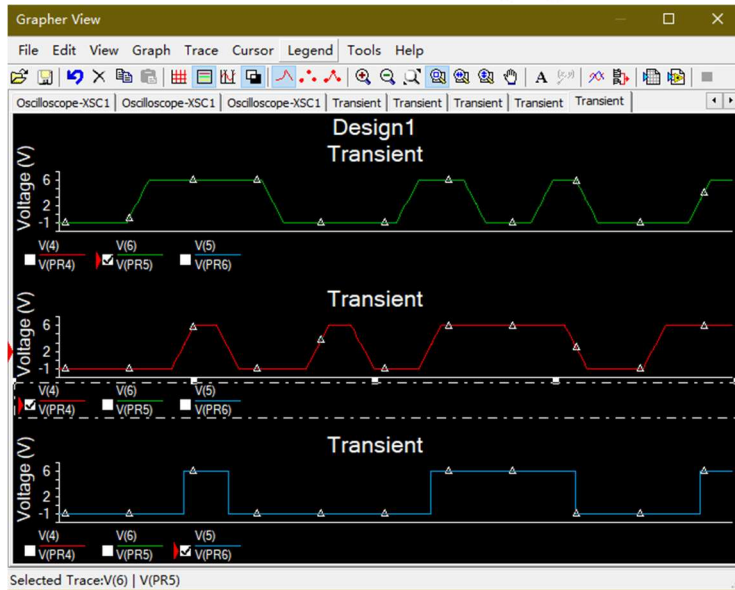 - Given the input waveforms shown in the following figure, sketch the output, Q, of a D latch. Check it out with Multisim and show the schematic and simulation result. (10')



** Please submit the softcopy of your solutions to the problems on gradescope.*

** All flow charts and codes should be enclosed in your solutions.*

** Discussion on methodology is allowed, yet, the assignment should be done individually. Plagiarism, once found, grades zero for the whole homework assignment!!*