





SI100B TUTORIAL-3

Misc.

Li Teng, Jiangting Xia, Haochuan Wan, Yiming Gao




Segment Display

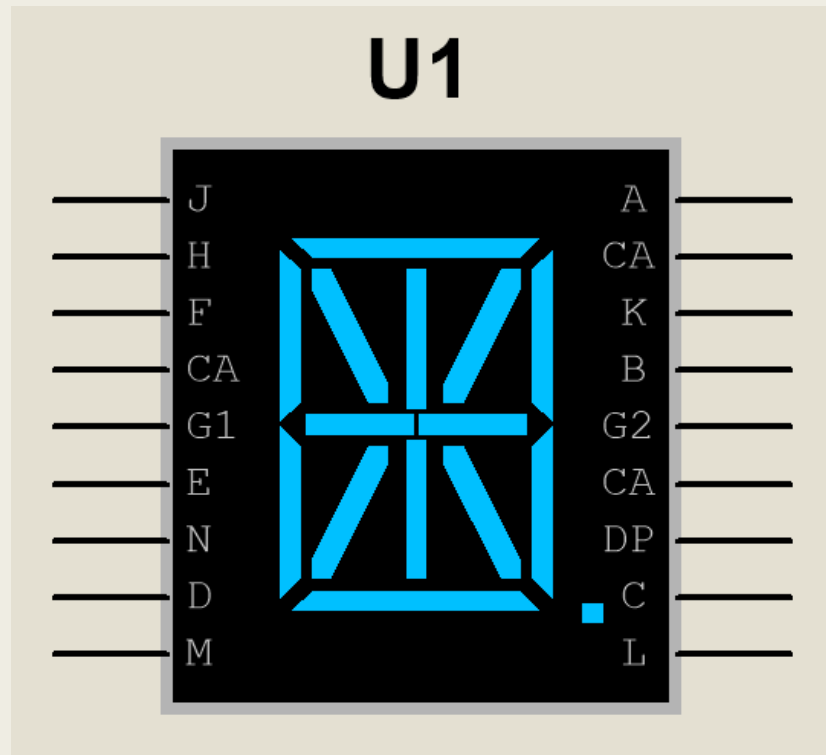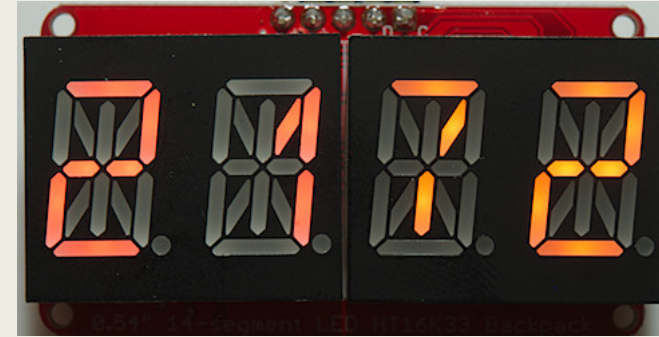



A-398X

4,13,17 CA


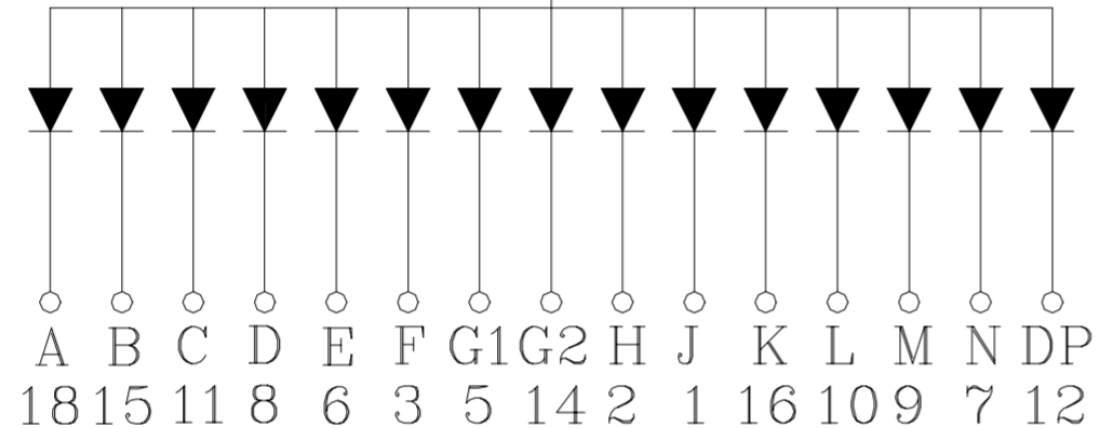


CA means "Common Anode". Connect it to VDD



Illumine “7”

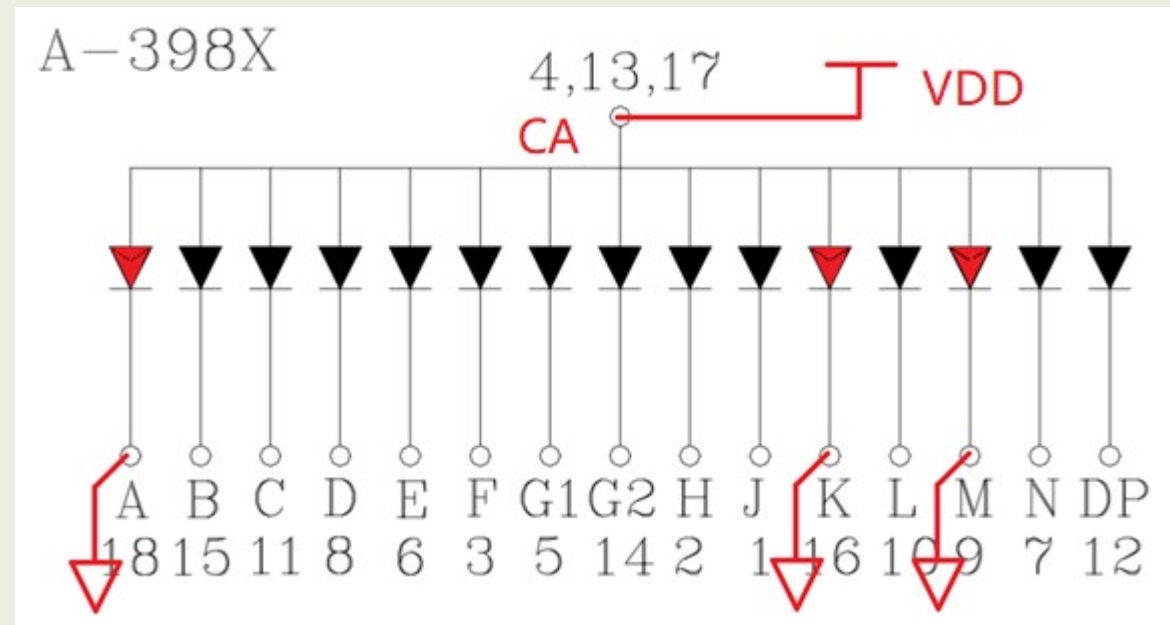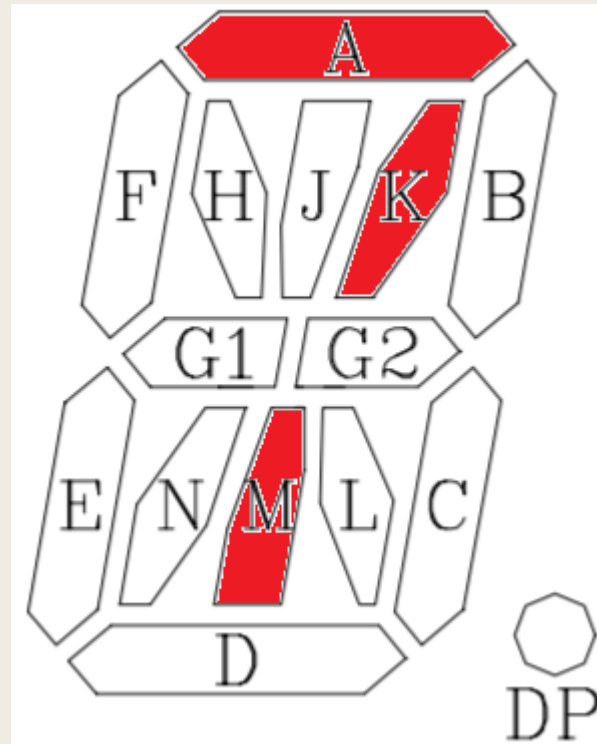


Illumine with Logic Gates

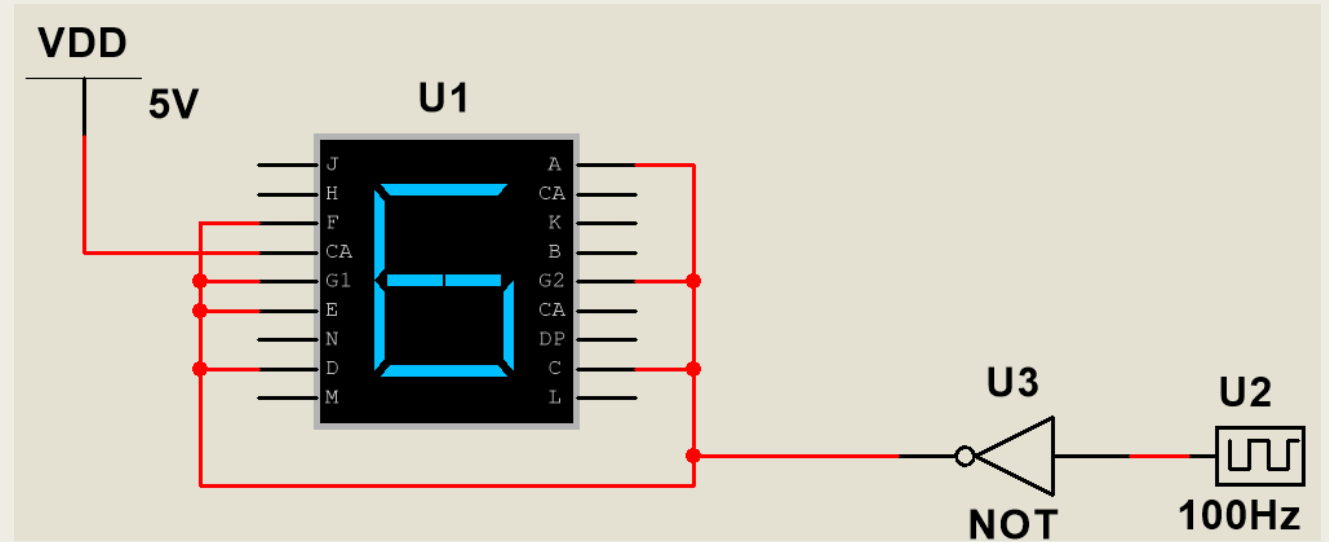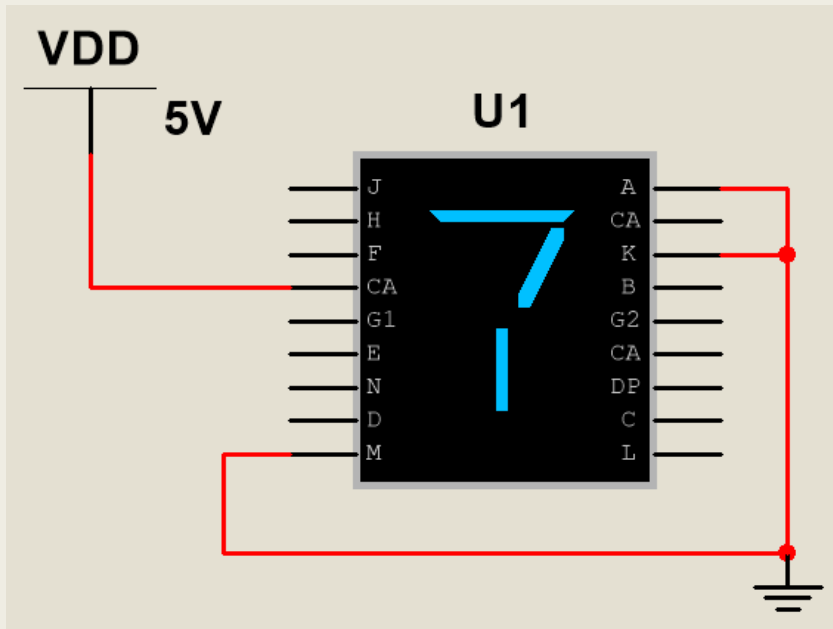


Finite-state Machine of Digital System

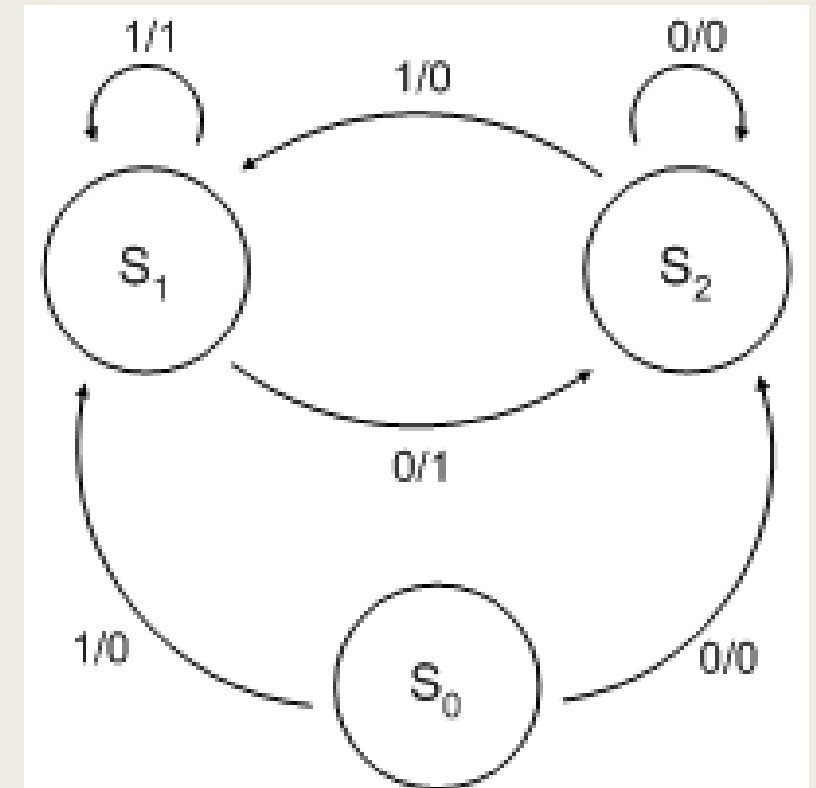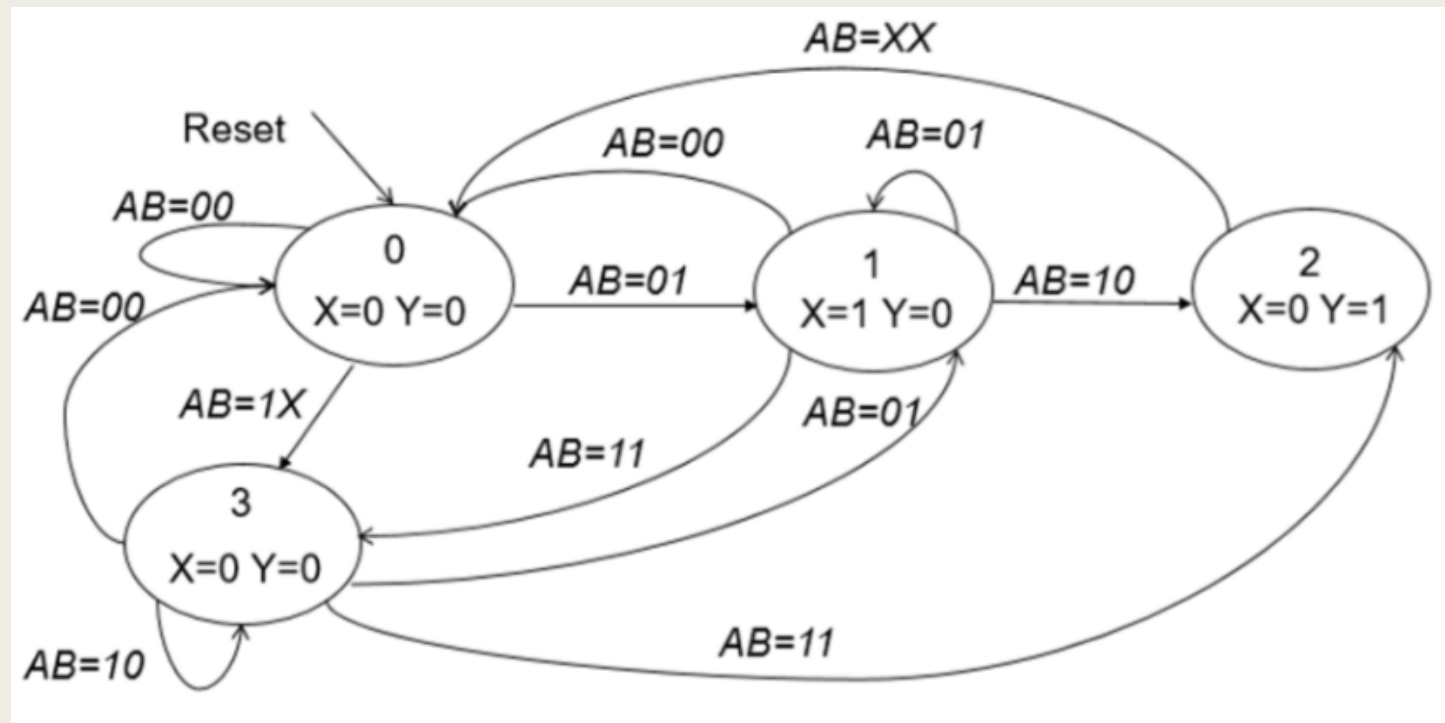


FSM of 🐱

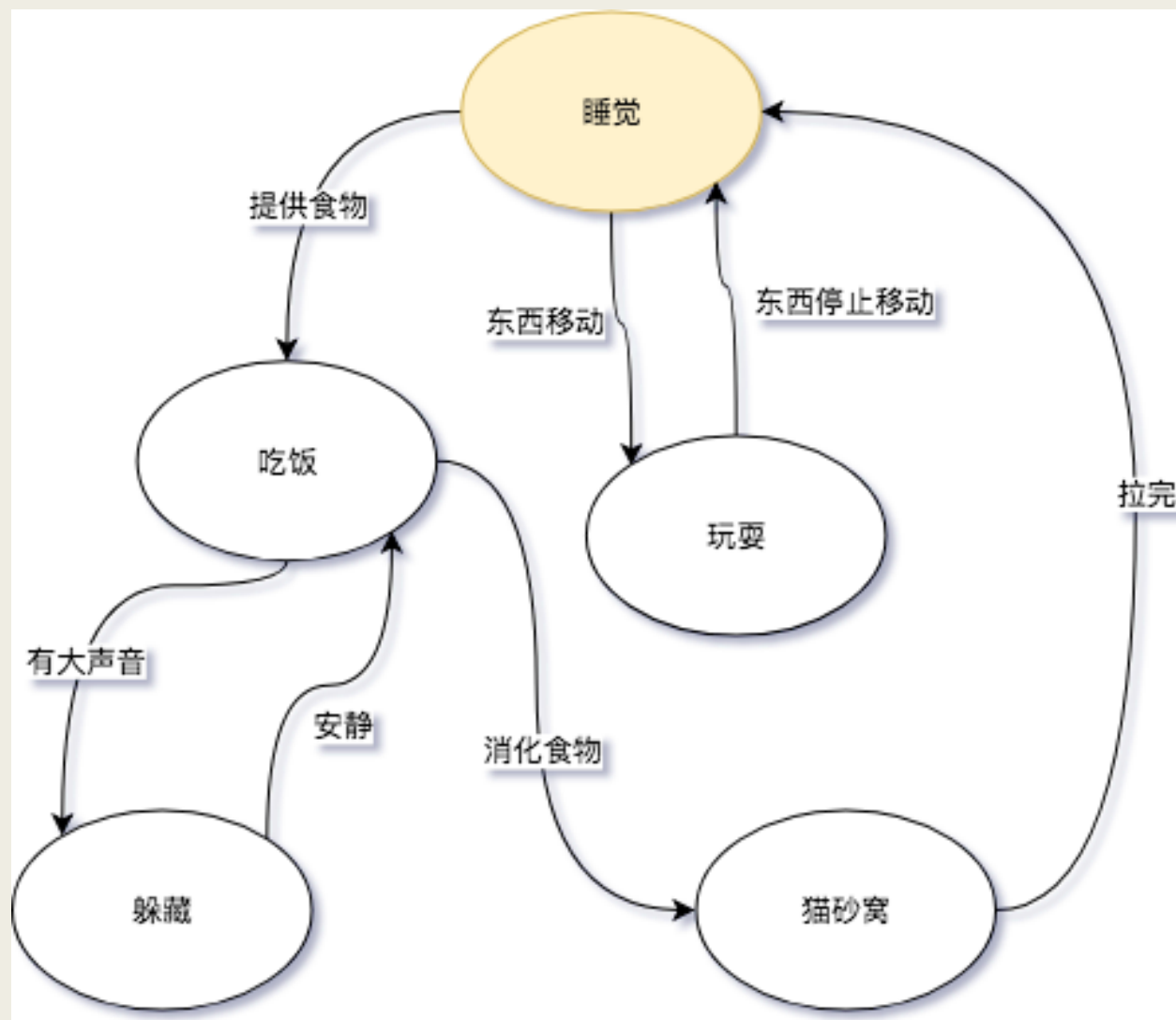

FSM of 🧑 or 🧒

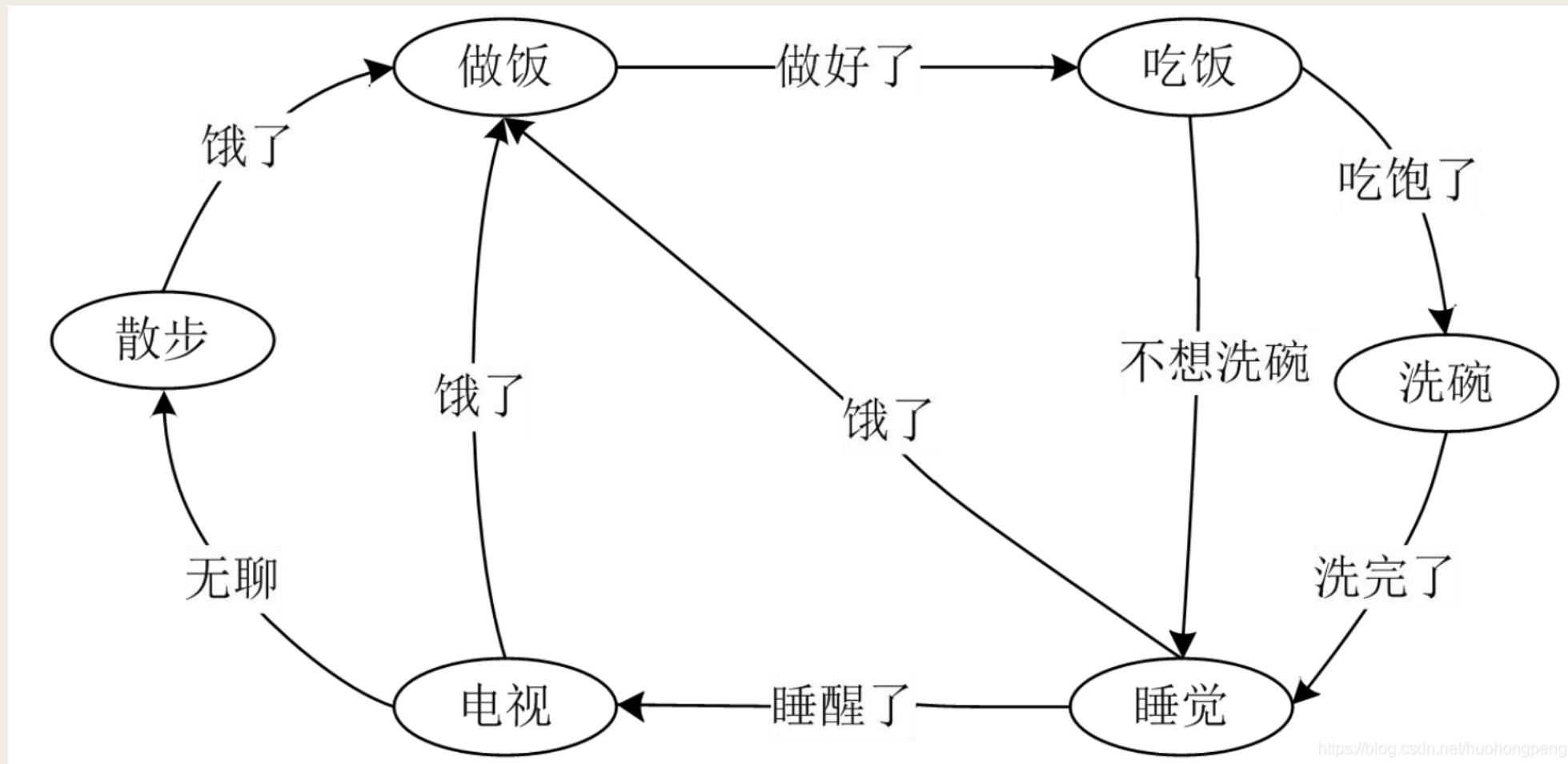

FSM in Action Games

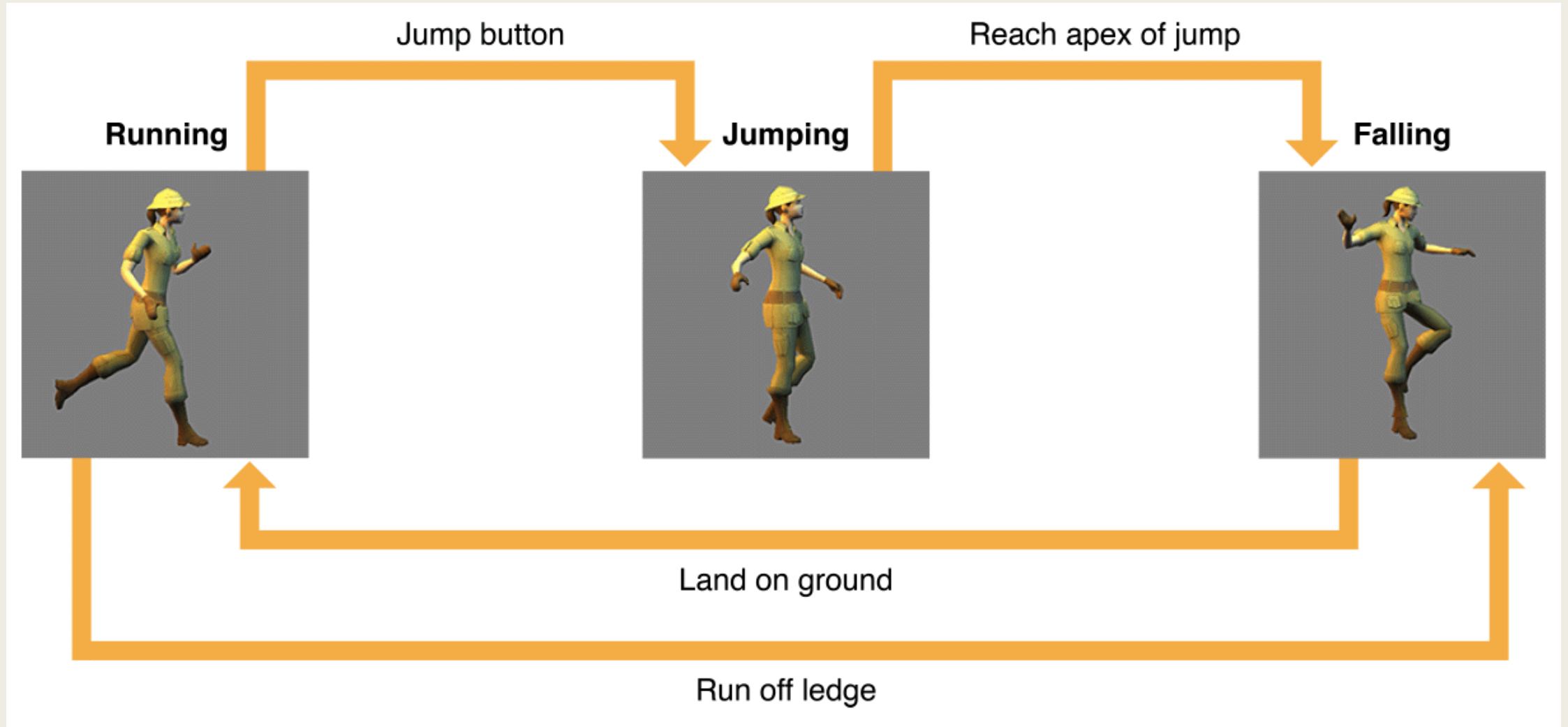



Motions in Video Games



危险动作，请勿模仿

FSM Design

0. 转换实际问题为状态机


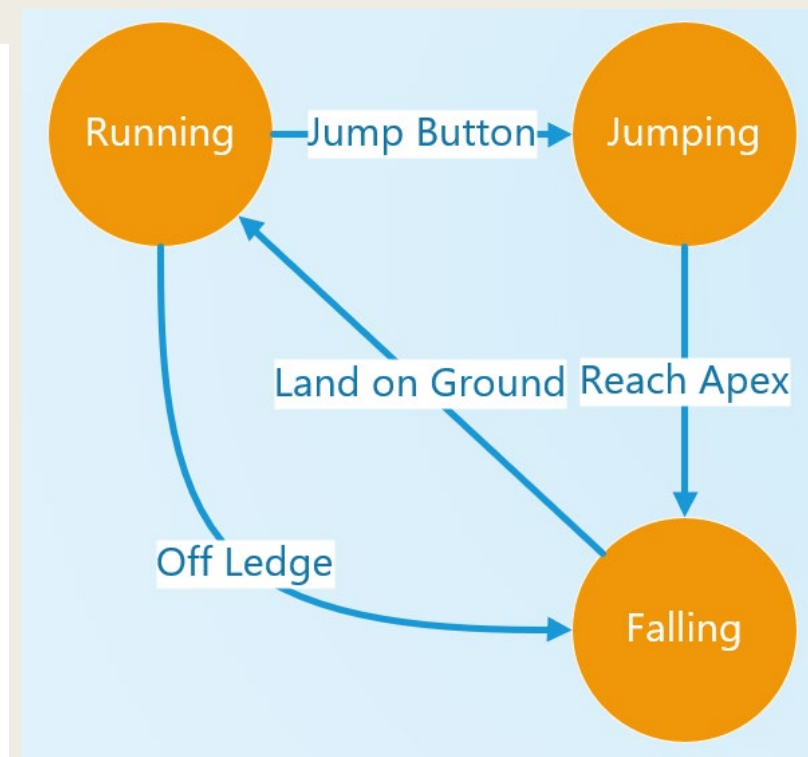
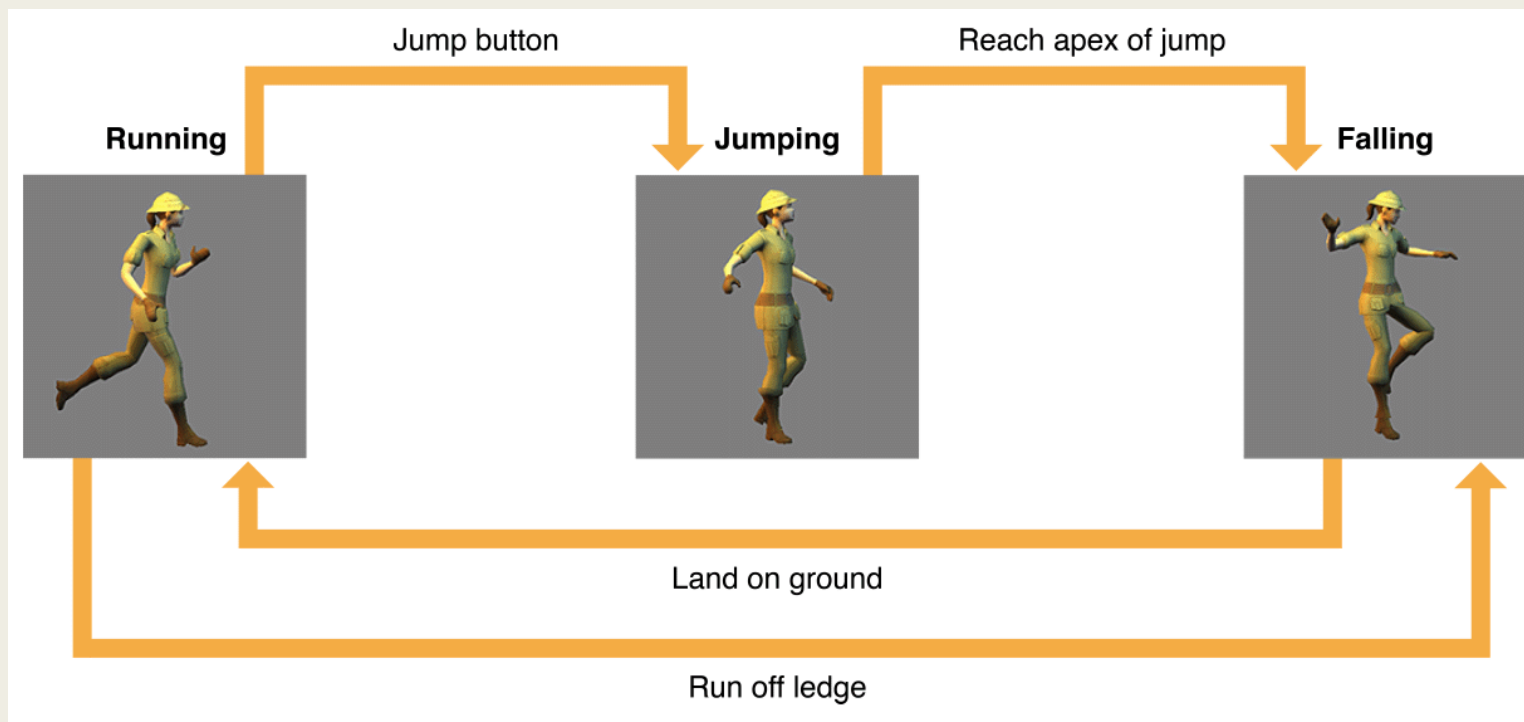


FSM Design

1. 状态编码&定义输入

	Binary Code(S1,S0)
Running	00
Jumping	01
Falling	10
Not Used	11


Input information	Definition
Jump button	A
Reach apex	B
Land on ground	C
Run off ledge	D

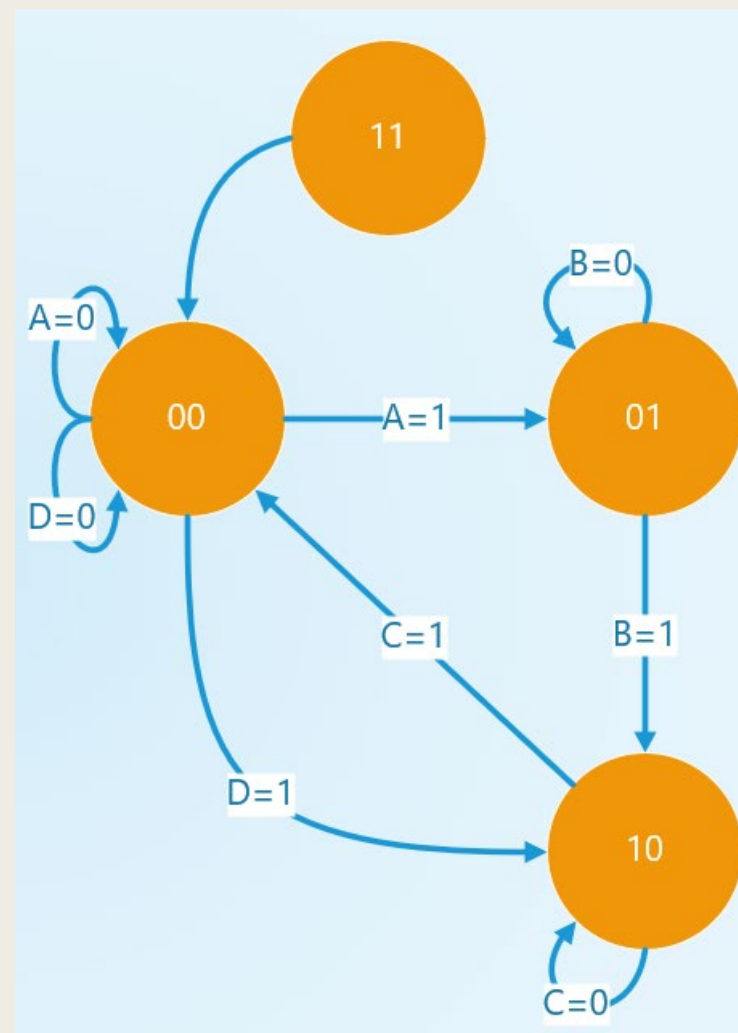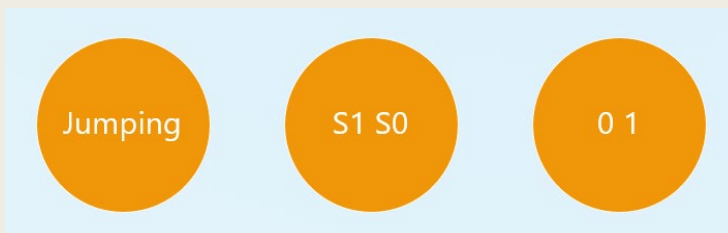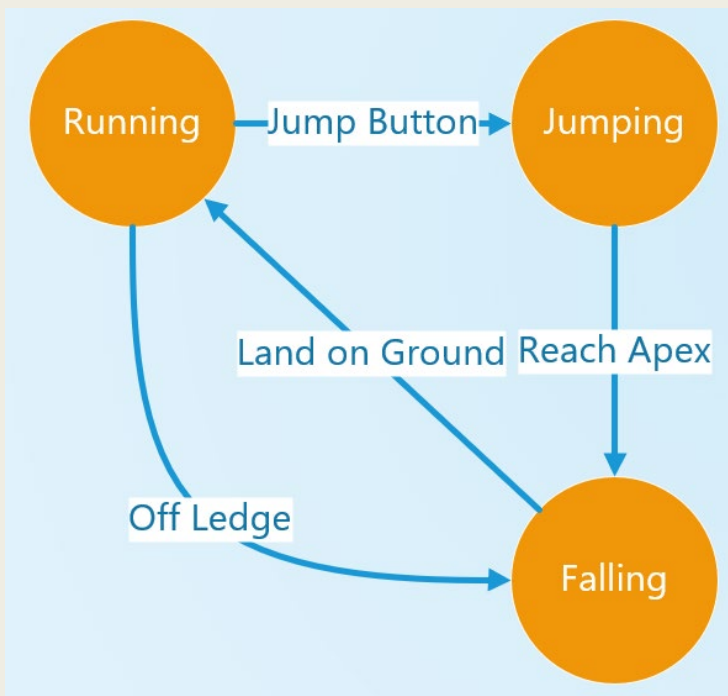

FSM Design

2. 列出状态转移表

S1	S0	A	B	C	D	S1*	S0*
0	0	1	x	x	x	0	1
0	0	0	x	x	x	0	0
0	0	x	x	x	1	1	0
0	0	x	x	x	0	0	0
0	1	x	1	x	x	1	0
0	1	x	0	x	x	0	1
1	0	x	x	1	x	0	0
1	0	x	x	0	x	1	0
1	1	x	x	x	x	0	0

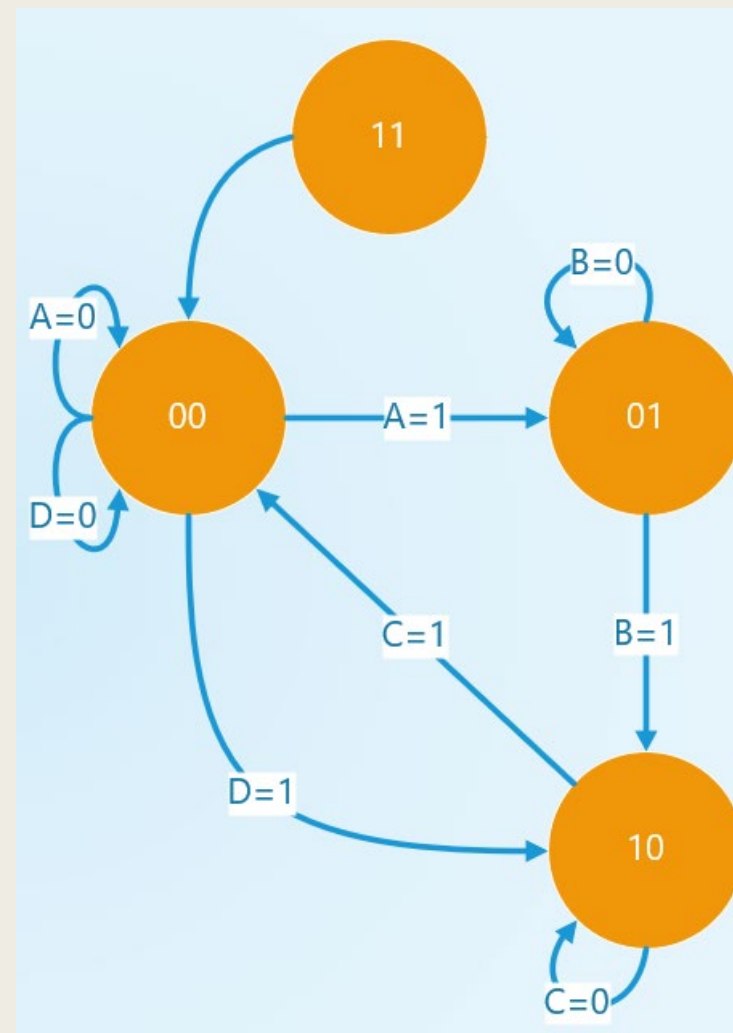

FSM Design

3. 列出转移方程

S1	S0	A	B	C	D	S1*	S0*
0	0	1	x	x	x	0	1
0	0	0	x	x	x	0	0
0	0	x	x	x	1	1	0
0	0	x	x	x	0	0	0
0	1	x	1	x	x	1	0
0	1	x	0	x	x	0	1
1	0	x	x	1	x	0	0
1	0	x	x	0	x	1	0
1	1	x	x	x	x	0	0

$$S_1^* = S_1'S_0'D + S_1'S_0B + S_1S_0'C'$$


$$S_0^* = S_1'S_0'A + S_1'S_0B'$$

FSM Design

4. 根据转移方程绘制时序电路


$$S_1^* = S_1'S_0'D + S_1'S_0B + S_1S_0'C'$$

$$S_0^* = S_1'S_0'A + S_1'S_0B'$$

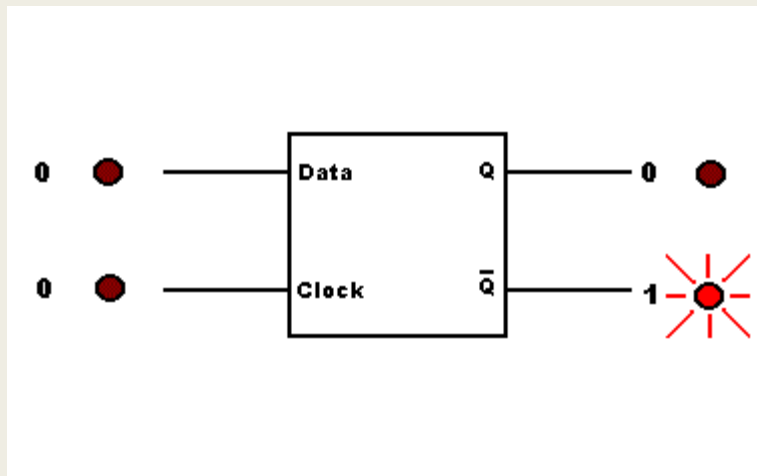

D Flip Flop (DFF)


Q	d	CK	Q*
x	0	↑	0
x	1	↑	1
0	X	else	0
1	X	else	1

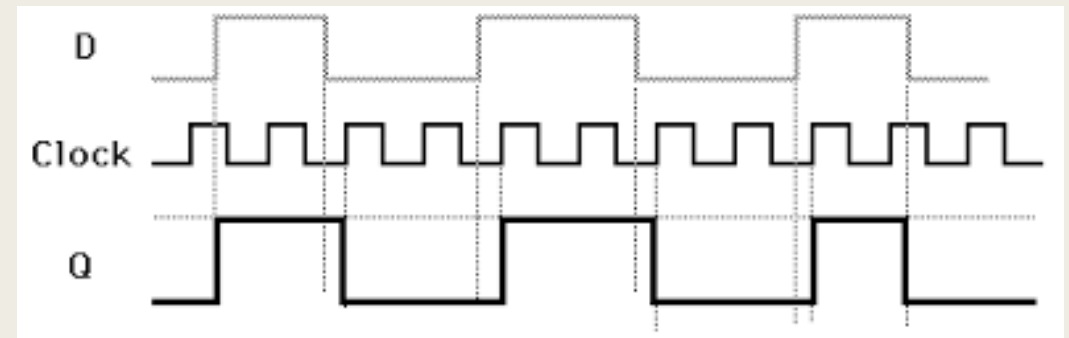

$$Q^* = d$$

FSM Design

5.设计输出电路(状态码转输出)

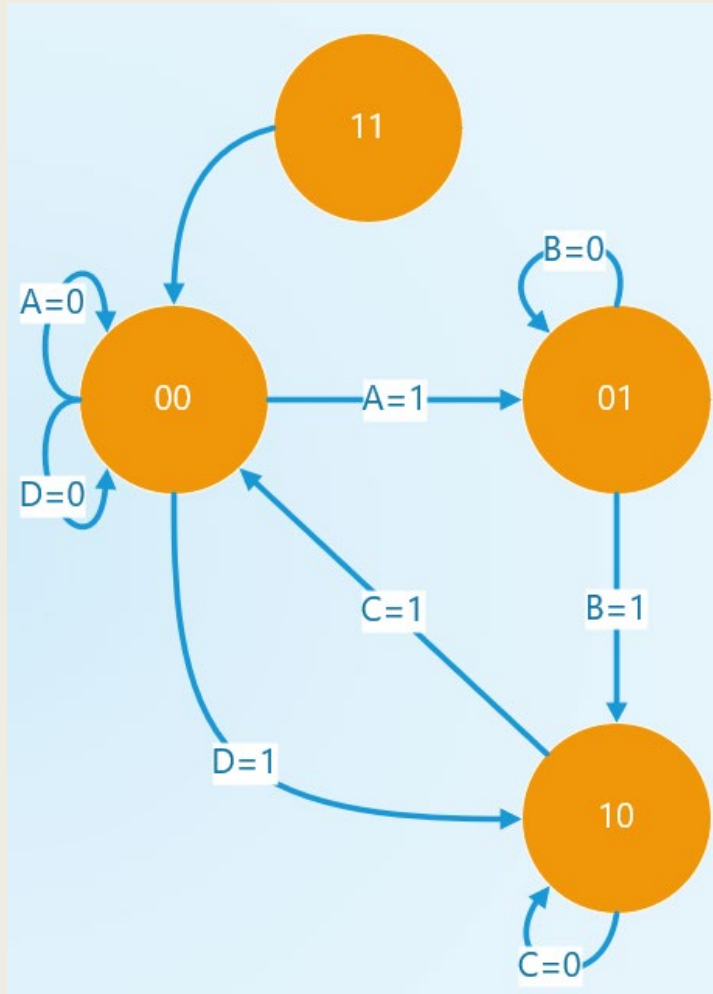

	Binary Code(S1,S0)
Running	00
Jumping	01
Falling	10
Not Used	11


$$\text{Running} = S_1'S_0'$$

$$\text{Jumping} = S_1'S_0$$


$$\text{Falling} = S_1S_0'$$

FSM Design

Final Circuit

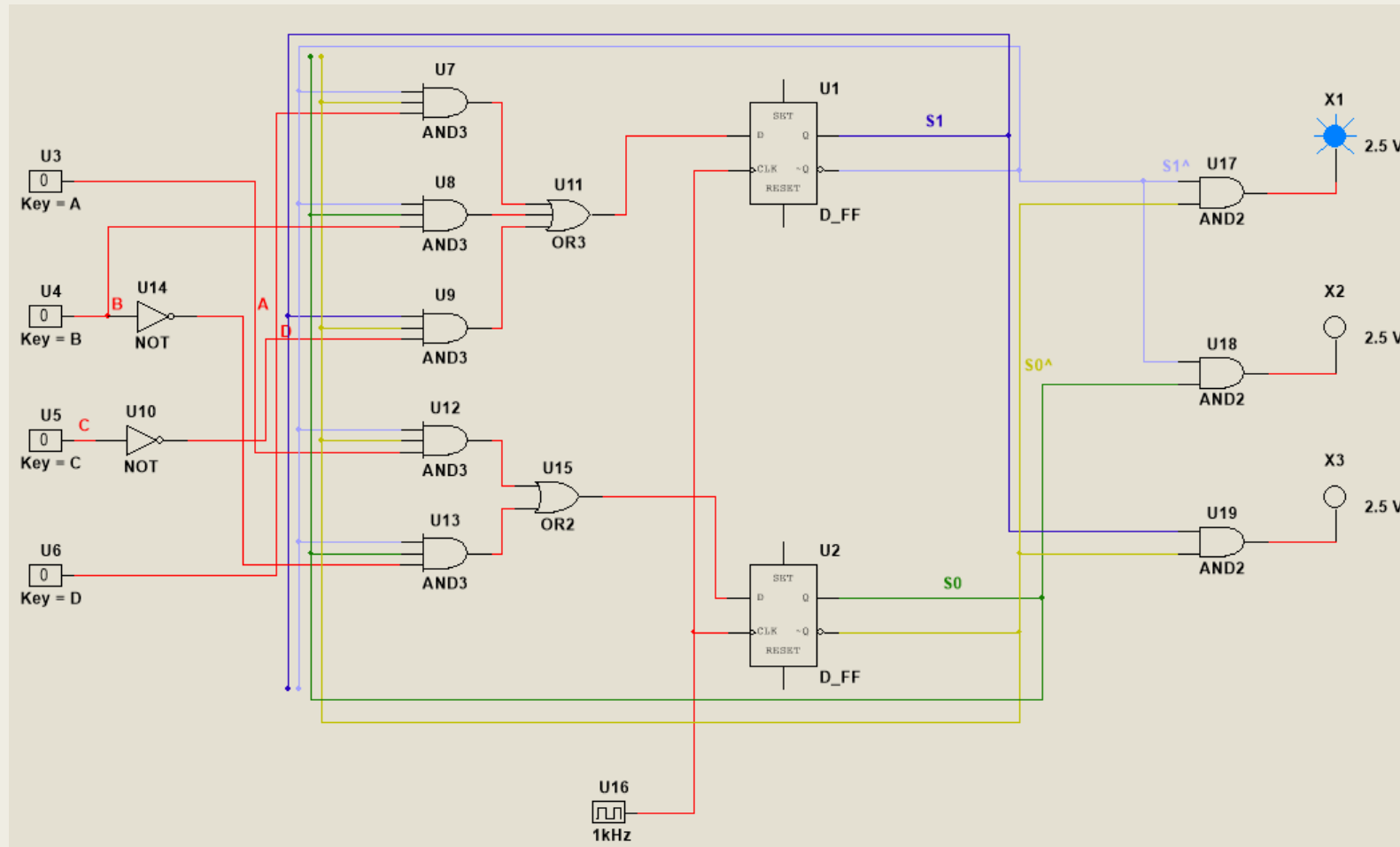

Potential Problem: Loops

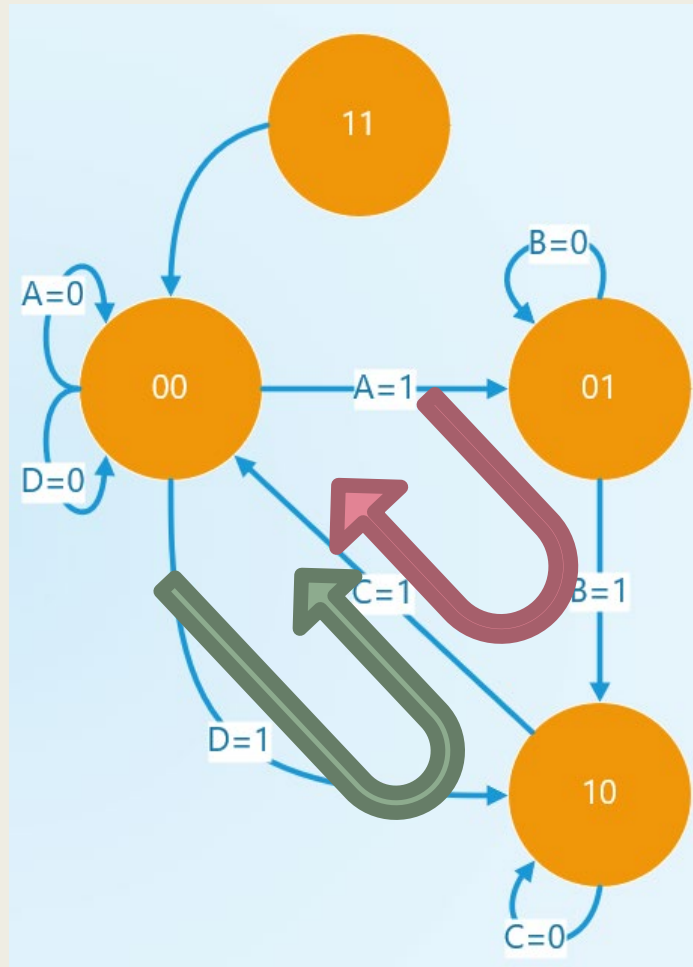

Thanks!