

SI100B


Introduction to Information Science and Technology (Part 3: Electrical Engineering)

Lecture #3 (Digital) Combinational Logic Circuits

Instructor: Junrui Liang (梁俊睿)

Nov. 13th, 2020

The Theme Story

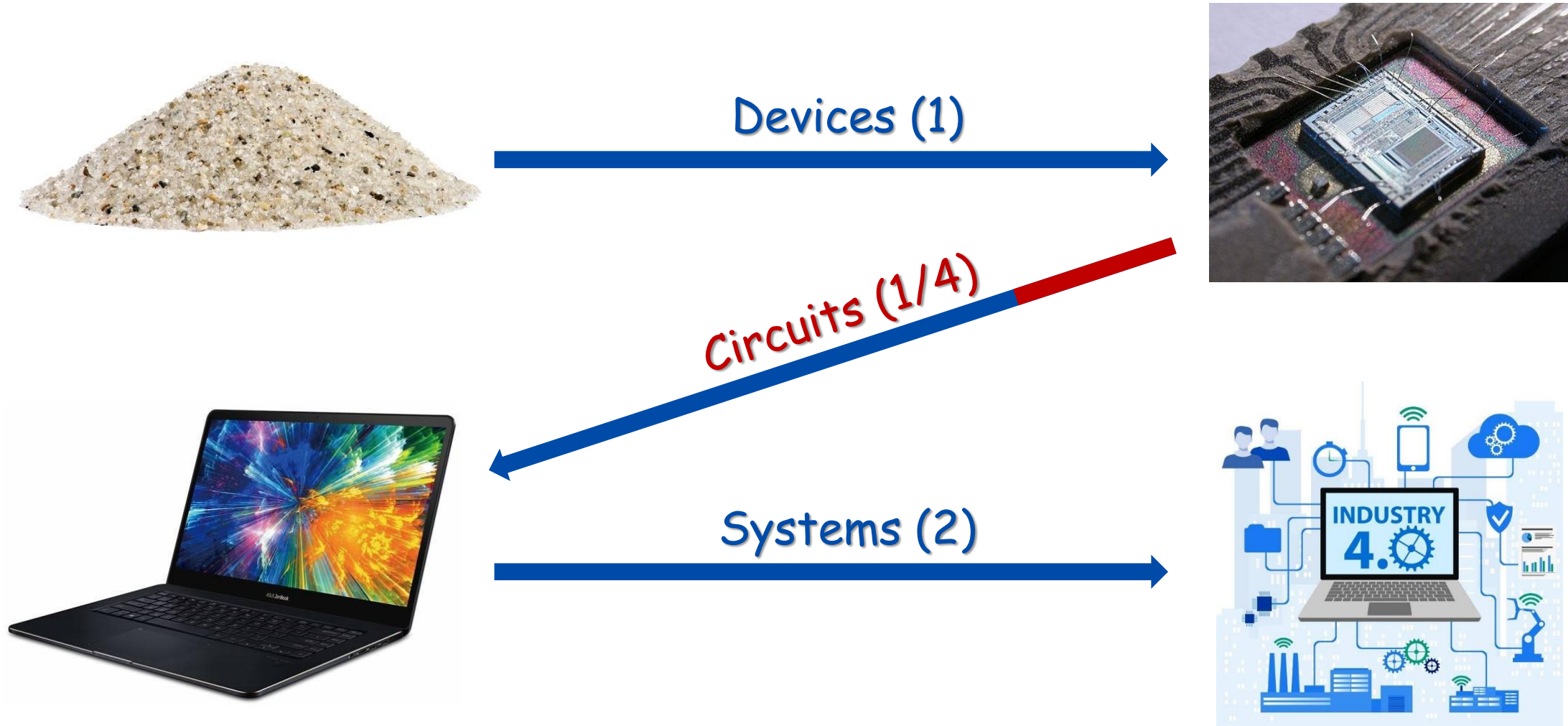

(Pictures are from the Internet)


Study Purpose of Lecture #3

- 哲学 (bao'an) 三问
 - Who are you?
 - Where are you from?
 - Where are you going?

To answer those questions
throughout your life



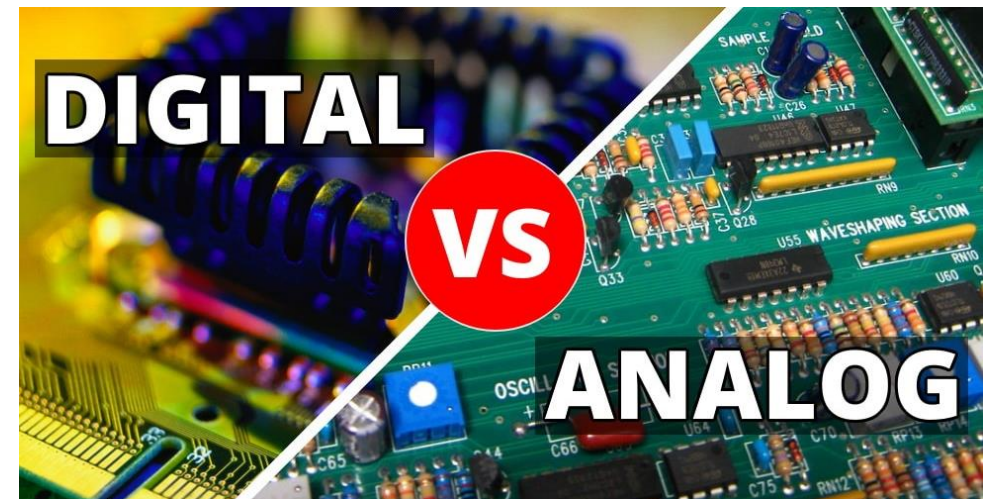- In this lecture, we ask
 - How many categories of circuits are there?
 - Why digital circuits 数字电路 won in computation & communication?
 - How to build combinational logic circuits 组合逻辑电路?




Lecture Outline

1. Circuit categories 电路种类
2. Boolean logic 布尔逻辑
3. Logic gates 逻辑门电路
4. Combinational logic circuit 组合逻辑电路
 - Example: majority circuit 投票选举电路实例

----- (break) -----

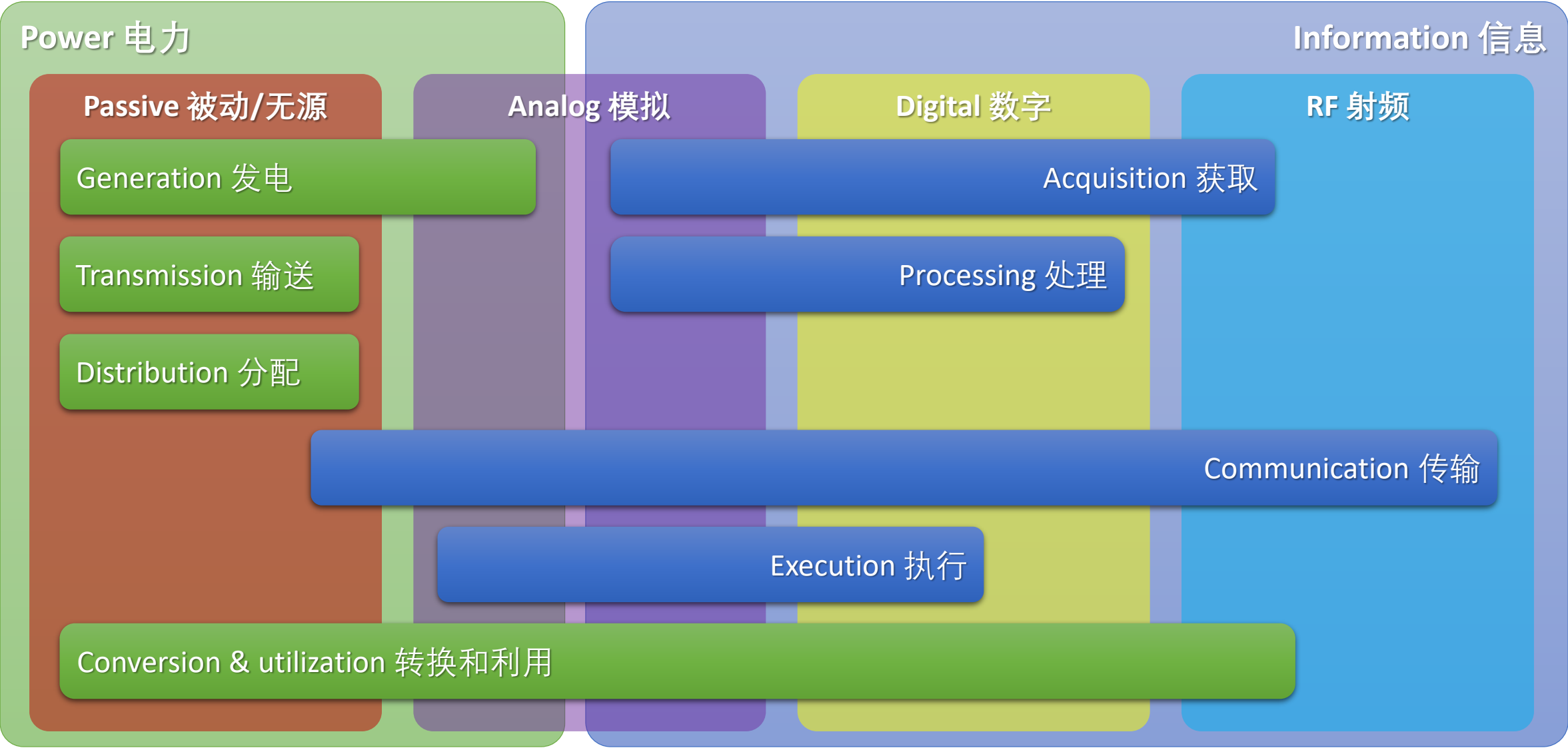
5. Combinational Logic Circuits Design 组合逻辑电路设计
 - Boolean algebra 布尔代数
 - Truth table 真值表
 - Karnaugh map 卡诺图
 - Example: seven-segment display decoder 七段码显示解码实例

Electrical circuits for different application purposes




Four typical circuit categories



• Passive 被动/无源

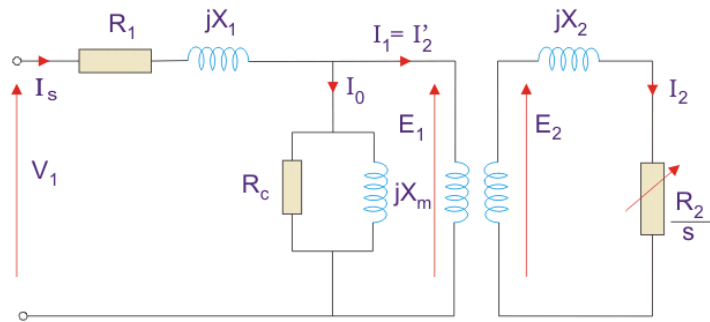



• Digital 数字

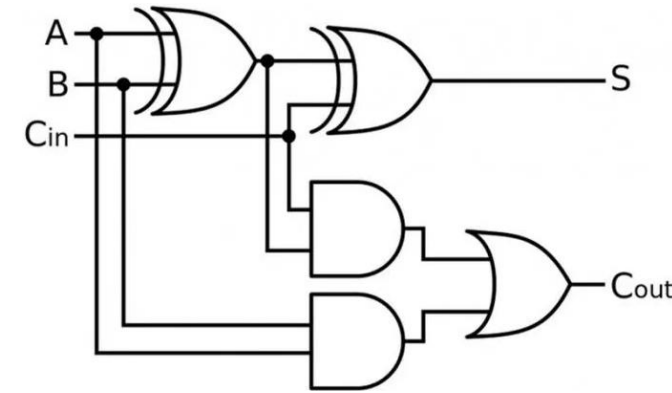

• Analog 模拟

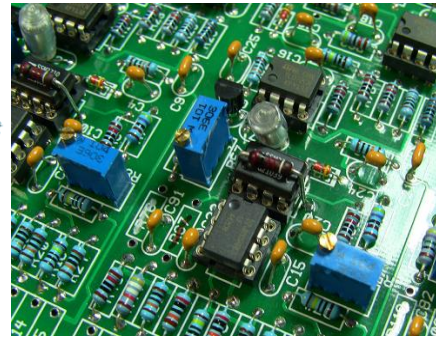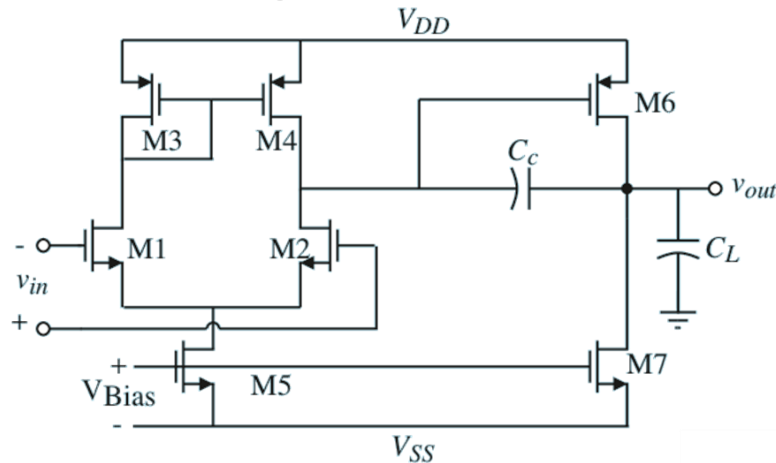


• RF 射频

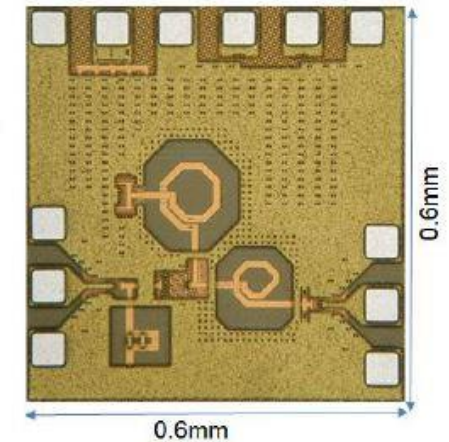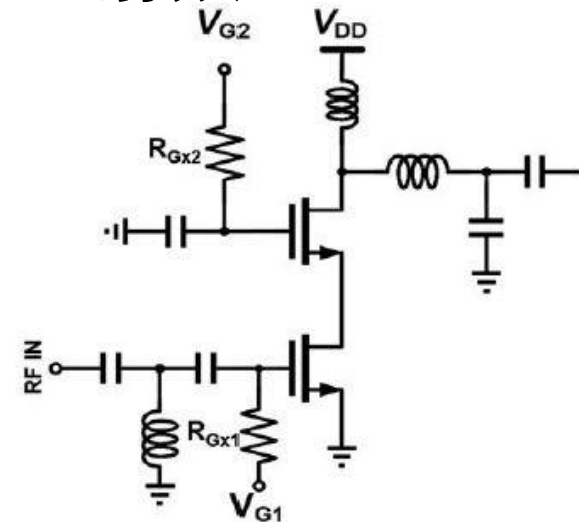

Boolean logic

- George Boole
(1815 - 1864)

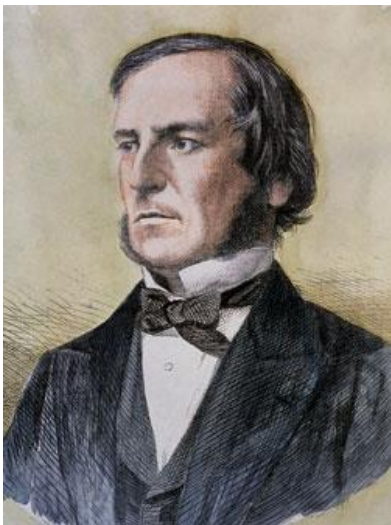


- Values


- Boolean algebra allows only two values—0 and 1
- The beauty of the *digital abstraction* is that digital designers can focus on 1's and 0's, ignoring whether the Boolean variables are physically represented with specific voltages, rotating gears, etc.

- Basic operations

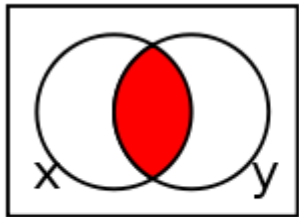- AND (conjunction) 与 xy
- OR (disjunction) 或 $x + y$
- NOT (negation) 非 \bar{x}



$x \wedge y$

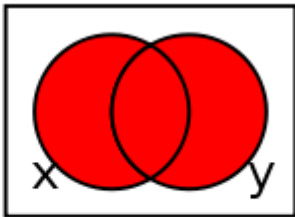

$x \vee y$



$\neg x$


Logic 0	Logic 1
False	True
Off	On
LOW	HIGH
No	Yes
Open switch	Closed switch

x	y	$x \wedge y$	$x \vee y$	x	$\neg x$
0	0	0	0	0	1
1	0	0	1	1	0
0	1	0	1		
1	1	1	1		

Basic logic gates

- NOT gate
- OR gate
- AND gate


NOT

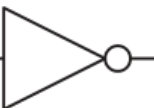

$Y = \bar{A}$

A	Y
0	1
1	0


OR



$Y = A + B$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1


AND

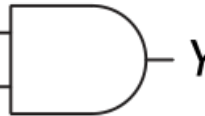

$Y = AB$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

AND4

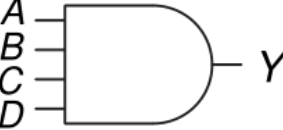


$Y = ABCD$

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

- Buffer

BUF


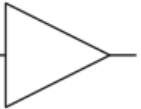


$Y = A$

A	Y
0	0
1	1

CMOS implementation of a buffer


• Why we need a buffer?

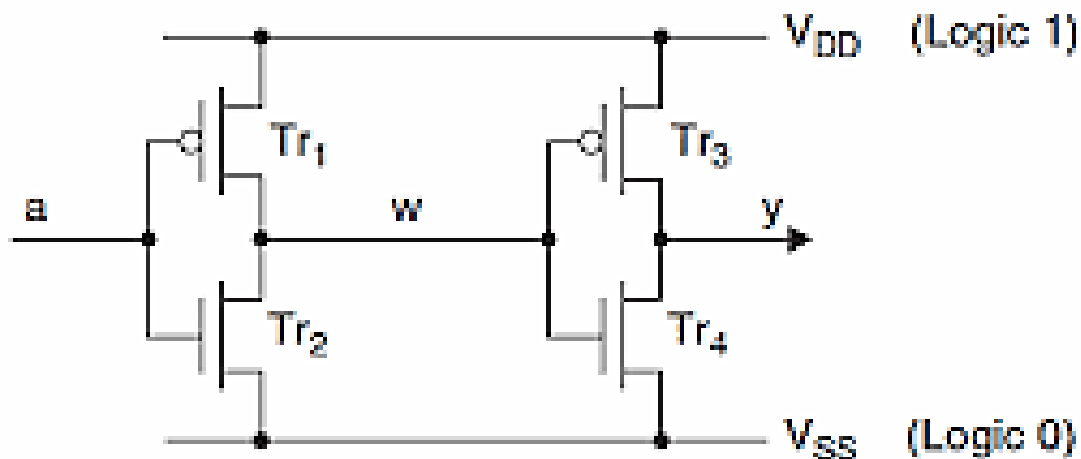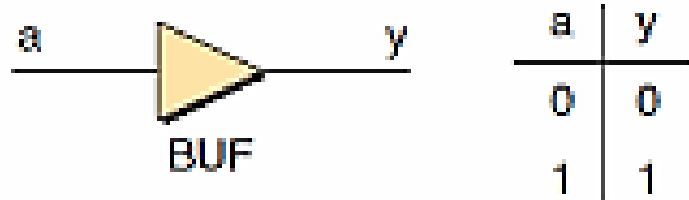


- From the logical point of view, a buffer might seem useless.
- From the analog point of view, the buffer might have desirable characteristics such as the ability to **deliver large amounts of current** to **drive** a motor or many gates.
- This is an example of why we **need to consider multiple levels of abstraction** to fully understand a system; the digital abstraction hides the real purpose of a buffer.

The physical considerations



- Noise margins

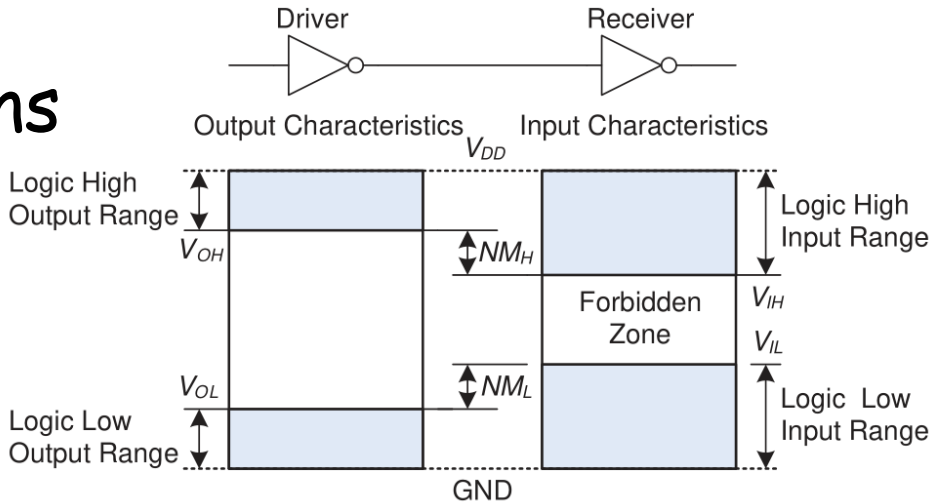


- DC transfer characteristics

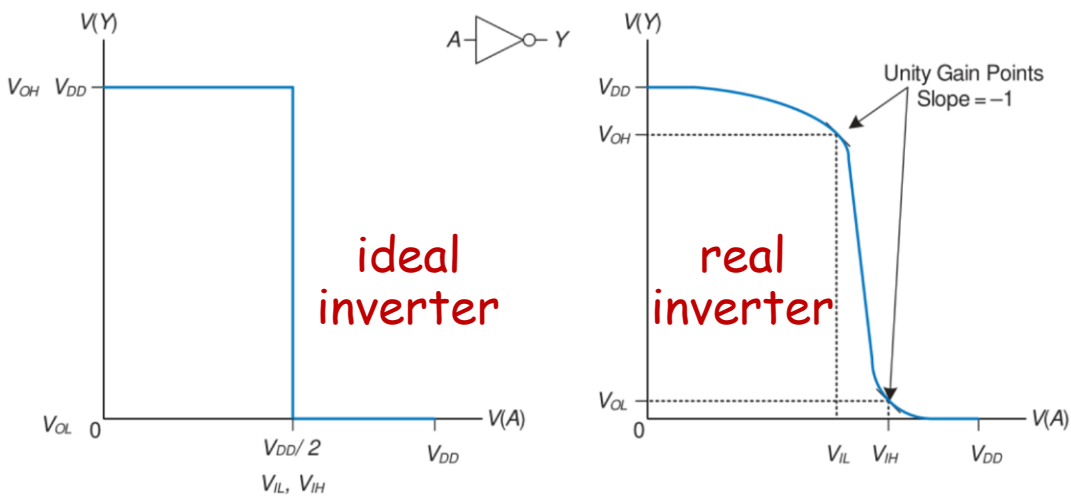

- Physical chip

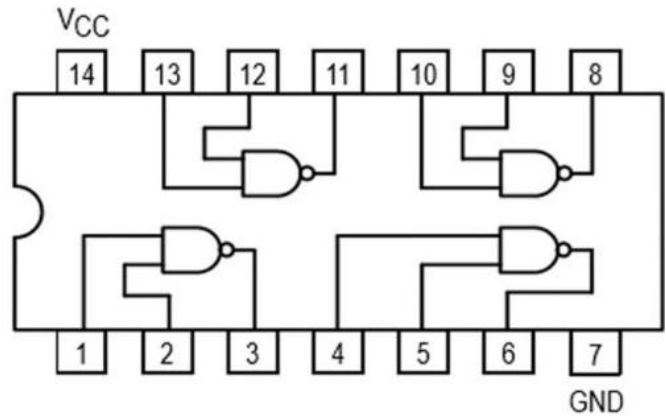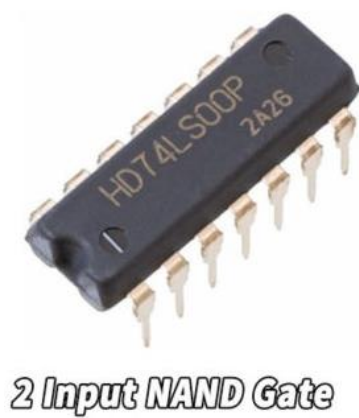

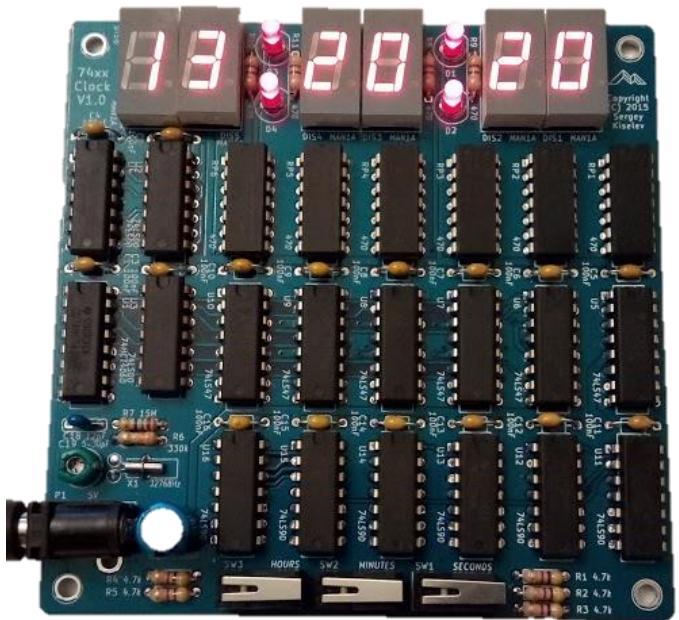- A digital clock built with 74LSxx chips



Other logic gates

异或门

XOR




$$Y = A \oplus B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

与非门

NAND

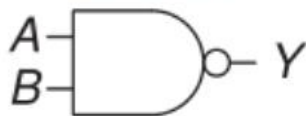

$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

或非门

NOR



$$Y = \overline{A + B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

同或门

XNOR



$$Y = \overline{A \oplus B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

三输入或非门

NOR3




$$Y = \overline{A + B + C}$$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Digital electronics

• Combinational logic circuit


组合逻辑

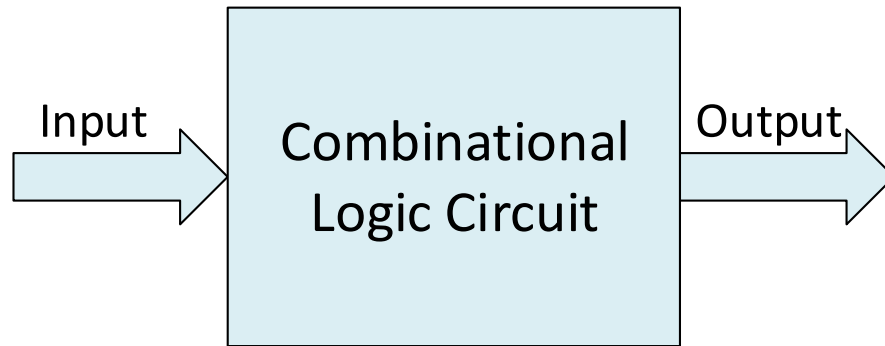

- Output depends on
 - Present input values
- No memory

• Sequential logic circuit

时序逻辑

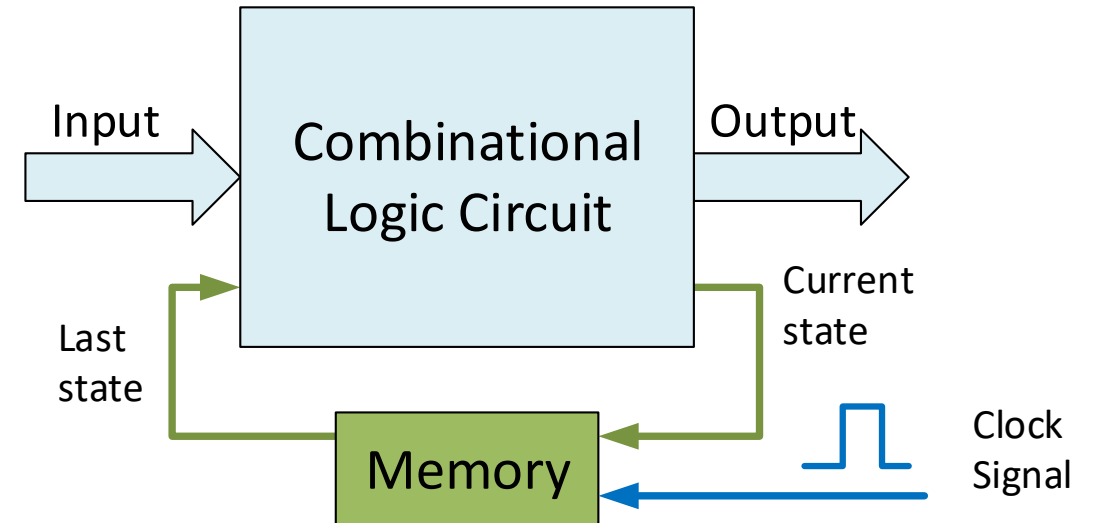

- Output depends on
 - Present inputs
 - The history of past inputs
- Have memory

Example: majority voting system

2020下半年最励志故事



看到74岁和77岁的两个老头，为了一份工作
争吵的这么激烈

好好学习信导课


你还有什么借口不努力呢？

Circuit implementation



- 3 input majority function
 - Truth table

S1	S2	S3	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

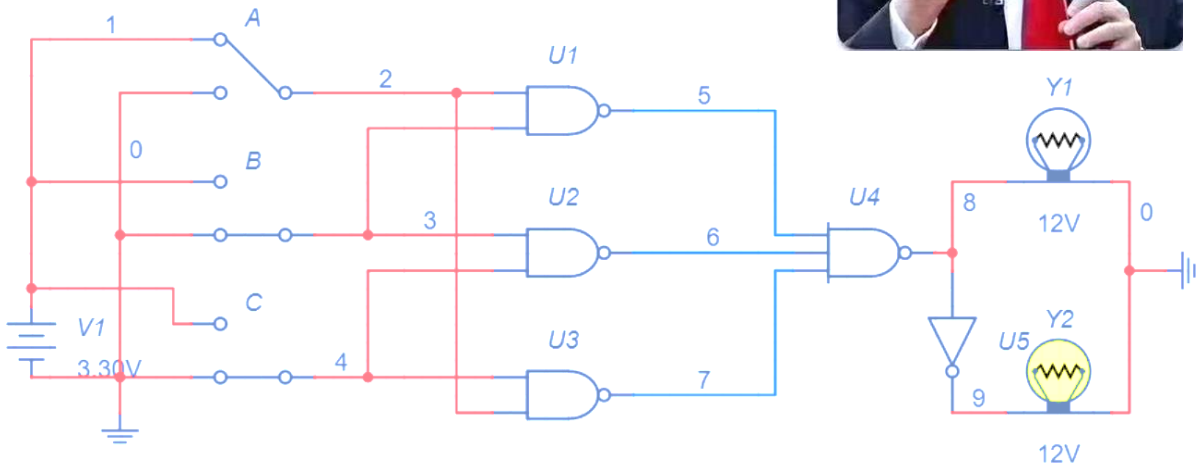

Why using NOR & NAND gates?

做的电路规模最小！！



- Logic expression

$$Y = AB + BC + AC$$
$$= \overline{\overline{AB} \overline{BC} \overline{AC}}$$

Boolean algebra

• Axioms 公理

Axiom		Dual		Name
A1	$B = 0 \text{ if } B \neq 1$	A1'	$B = 1 \text{ if } B \neq 0$	Binary field
A2	$\overline{0} = 1$	A2'	$\overline{1} = 0$	NOT
A3	$0 \bullet 0 = 0$	A3'	$1 + 1 = 1$	AND/OR
A4	$1 \bullet 1 = 1$	A4'	$0 + 0 = 0$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	A5'	$1 + 0 = 0 + 1 = 1$	AND/OR

• Theorems of two variables

Theorem		Dual		Name
T6	$B \bullet C = C \bullet B$	T6'	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	T7'	$(B + C) + D = B + (C + D)$	Associativity
T8	$(B \bullet C) + (B \bullet D) = B \bullet (C + D)$	T8'	$(B + C) \bullet (B + D) = B + (C \bullet D)$	Distributivity
T9	$B \bullet (B + C) = B$	T9'	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \overline{C}) = B$	T10'	$(B + C) \bullet (B + \overline{C}) = B$	Combining
T11	$(B \bullet C) + (\overline{B} \bullet D) + (C \bullet D) = B \bullet C + \overline{B} \bullet D$	T11'	$(B + C) \bullet (\overline{B} + D) \bullet (C + D) = (B + C) \bullet (\overline{B} + D)$	Consensus
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots} = (\overline{B_0} + \overline{B_1} + \overline{B_2} \dots)$	T12'	$\overline{B_0 + B_1 + B_2 \dots} = (\overline{B_0} \bullet \overline{B_1} \bullet \overline{B_2} \dots)$	De Morgan's Theorem

• Theorems of one variable

Theorem		Dual		Name
T1	$B \bullet 1 = B$	T1'	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	T2'	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	T3'	$B + B = B$	Idempotency
T4		$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	T5'	$B + \overline{B} = 1$	Complements

Generalized procedures of combinational circuit design

- Improved equation minimization

Step	Equation	Justification
	$\overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C} + A \overline{B} C$	
1	$\overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C} + A \overline{B} \overline{C} + A \overline{B} C$	T3: Idempotency
2	$\overline{B} \overline{C}(\overline{A} + A) + A \overline{B}(\overline{C} + C)$	T8: Distributivity
3	$\overline{B} \overline{C}(1) + A \overline{B}(1)$	T5: Complements
4	$\overline{B} \overline{C} + A \overline{B}$	T1: Identity

OK
• Sum of product 积(与)的和(或)
(Multiple AND terms ORed together)

- 1. $ABC + \overline{A} \overline{B} \overline{C}$
- 2. $AB + \overline{A} \overline{B} \overline{C} + \overline{C} \overline{D} + D$
- 3. $\overline{A} B + \overline{C} \overline{D} + EF + GK + H \overline{L}$

化简!
• Product of sum 和(或)的积(与)
(Multiple OR terms ANDed together)

- 1. $(A + \overline{B} + C)(A + C)$
- 2. $(A + \overline{B})(\overline{C} + D)F$
- 3. $(A + C)(B + \overline{D})(\overline{B} + C)(A + \overline{D} + \overline{E})$

Generalized procedures of combinational circuit design



- Interpret the problem and set up its **truth table**
- Write the **AND** (product) **term** for each case where output = 1
- Combine the terms in **SOP** (sum of product) form 先与再或的形式
- **Simplify** the output expression if possible
- Implement the **circuit** for the final, simplified expression

• Equation minimization example

Step	Equation	Justification
	$\bar{A} \bar{B} \bar{C} + A \bar{B} \bar{C} + A \bar{B} C$	
1	$\bar{B} \bar{C}(\bar{A} + A) + A \bar{B} C$	T8: Distributivity
2	$\bar{B} \bar{C}(1) + A \bar{B} C$	T5: Complements
3	$\bar{B} \bar{C} + A \bar{B} C$	T1: Identity

Generalized procedures of combinational circuit design

- Improved equation minimization

Step	Equation	Justification
	$\overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C}$	
1	$\overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C}$	T3: Idempotency
2	$\overline{B} \overline{C}(\overline{A} + A) + A \overline{B}(\overline{C} + C)$	T8: Distributivity
3	$\overline{B} \overline{C}(1) + A \overline{B}(1)$	T5: Complements
4	$\overline{B} \overline{C} + A \overline{B}$	T1: Identity

Karnaugh map (K-maps)

- A graphical method for simplifying Boolean equations

- Invented in 1953 by **Maurice Karnaugh** at Bell Labs
- Adjacent squares share all the same literals **except one**
相邻格的输入值**仅有一位变化**
- The K-map also "**wraps around**."
左右环接

!important

		BC			
		00	01	11	10
A	0	1	0	1	1
	1	1	0	0	1

尽可能大的圈

包住1
(不一定要所有)

圈的大小只能是

1 2 4 8 ...

圈可以重叠

- Rules for finding a minimized equation :

- Use the **fewest circles** necessary to cover all the 1's.
- All the squares in each circle **must contain 1's**.



Each circle must span a **rectangular block** that is a power of 2 (i.e., 1, 2, or 4) squares in each direction.

- Each circle should be **as large as possible**.
- A circle may **wrap around** the edges of the K-map.
- A 1 in a K-map **may be circled multiple times** if doing so allows fewer circles to be used.

此图代表 $\bar{C} + \bar{A}B$

Example: 7-segment decoder

- 7-segment display

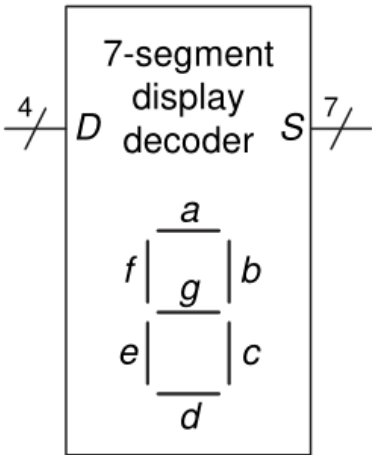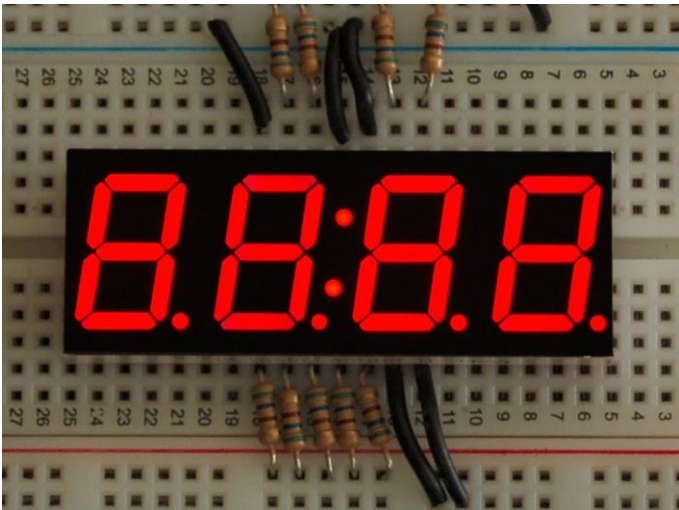

- Truth table


binary-coded decimal (BCD)

<i>D</i> _{3:0}	<i>S</i> _{<i>a</i>}	<i>S</i> _{<i>b</i>}	<i>S</i> _{<i>c</i>}	<i>S</i> _{<i>d</i>}	<i>S</i> _{<i>e</i>}	<i>S</i> _{<i>f</i>}	<i>S</i> _{<i>g</i>}
0000	1	1	1	1	1	1	0
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1	1	1	0	0	1
0100	0	1	1	0	0	1	1
0101	1	0	1	1	0	1	1
0110	1	0	1	1	1	1	1
0111	1	1	1	0	0	0	0
1000	1	1	1	1	1	1	1
1001	1	1	1	0	0	1	1
others	0	0	0	0	0	0	0




Example: 7-segment decoder

• K-map solution of S_a

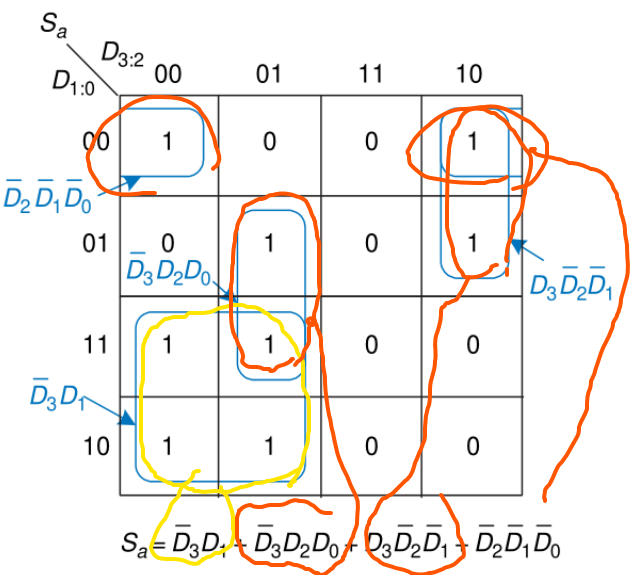

Alternative K-map

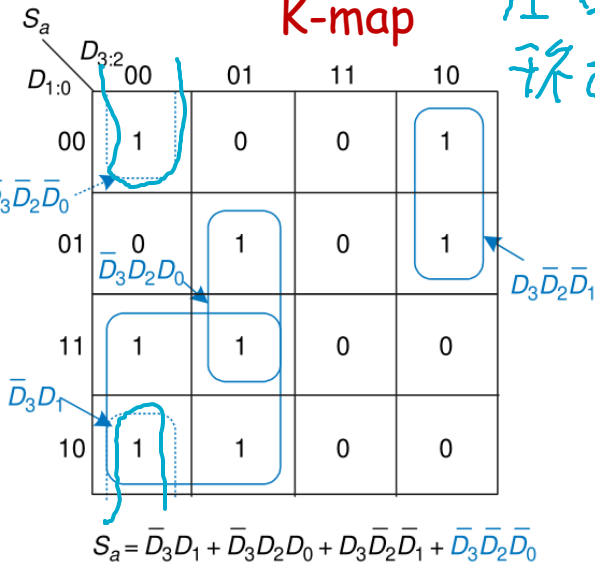

• Truth table

$D_{3:0}$	S_a	S_b	S_c	S_d	S_e	S_f	S_g
0000	1	1	1	1	1	1	0
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1	1	1	0	0	1
0100	0	1	1	0	0	1	1
0101	1	0	1	1	0	1	1
0110	1	0	1	1	1	1	1
0111	1	1	1	0	0	0	0
1000	1	1	1	1	1	1	1
1001	1	1	1	0	0	1	1
others	0	0	0	0	0	0	0

• Result & circuit

